

TOWARDS HIGHLY EFFICIENT MONOLITHIC DC/DC CONVERTER

Piyush Keshri
3rd Year Undergraduate Student
Indian Institute of Technology Kanpur, India
Tutor: Prof. Heiner Rysel

Outline

- Introduction
- Types of Switching Regulators
 - ❑ Buck Converter
 - ❑ Modes of operation of Buck converter
 - ❑ Boost converter
- Structure of monolithic Converter
- Method of operation of various parts of the converter.
- Integration of Inductor on chip
- Integration of capacitor on chip
- Power losses in the converter
- Power flow analysis
- Issues in monolithic DC/DC converter
- Techniques to improve performance
 - ❑ Compensated Error amplifier
 - ❑ Light load efficiency


Introduction

What is DC/DC Converter?

- A device that accepts a DC input voltage
- Produces a DC output voltage
- **Used to provide:**
 - ❑ Noise isolation
 - ❑ Power bus regulation etc.
 - ❑ Output at different voltage level
 - ❑ Wide Input voltage range
 - ❑ Constant Output Voltage
 - ❑ Galvanic Isolation

Linear Regulator

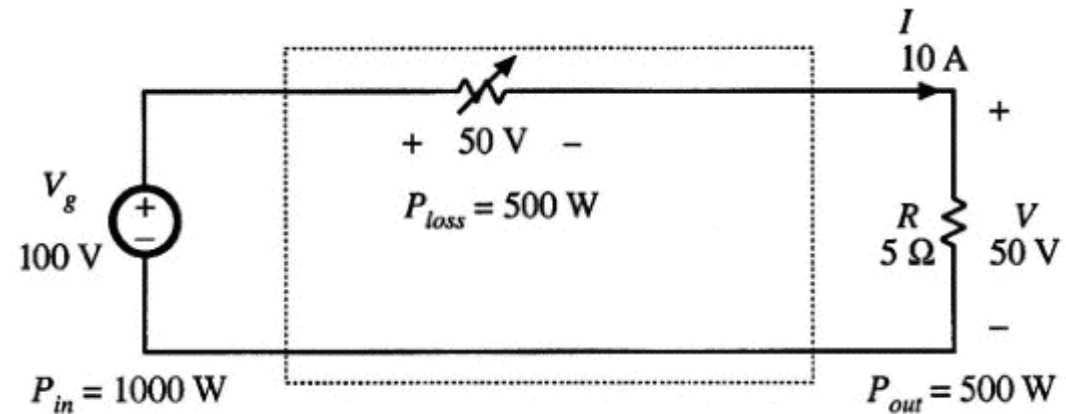- Extremely inefficient (depending on voltage drop!)
- High heat dissipation
- Bulky and expensive heat sink
- Impossible for SOC design
- Reduce battery life
- No switching noise



Switching Regulator

- Takes small chunk of energy from i/p & transfer to the o/p
- Uses electrical switch & controller to regulate rate of energy
- High efficiency
- Used in portable devices- cell phones, laptops, robots etc.
- Smaller size
- Lower heat generation
- Suitable for on chip design

Disadvantages of Switching Regulator

- Complex System Design
- High frequency electrical noise
- Ripple voltage at switching frequency

 


Fig. Buck Converter.

Types of Switch Mode Regulators

- Buck Converter- Step-down converter
- Boost Converter- Step-up converter
- Cuk Converter
- Isolated converters:
 - Flyback converter
 - Forward converter
 - Full- / Half bridge converter

 


Fig. Flyback Converter.

 


Fig. Buck Converter.

 


Fig. Boost Converter.

 


Fig. Cuk Converter.

Buck Converter

When Transistor 'ON'

- Inductor current rises

When Transistor 'OFF'

- Current through inductor passes through the diode

Modes of operation:

- Continuous Mode
- Transition b/w Continuous & Discontinuous Mode
- Discontinuous Mode

 


Fig. Circuit Layout Of Buck Converter

Buck Converter

Continuous Mode

Now, $V_x - V_o = L \frac{di}{dt}$



The change in current satisfies,

$$di = \int_{ON} (V_x - V_o) dt + \int_{OFF} (V_x - V_o) dt$$

For steady state operation,

$$di = 0 = \int_{ON} (V_x - V_o) dt + \int_{OFF} (V_x - V_o) dt$$

  Hence, $\frac{V_o}{V_{in}} = \frac{ton}{T}$



Buck Converter

Transition b/w Continuous & Discontinuous Mode

➤ Inductor current just goes to zero.

Now, during the ON time $V_{in} - V_{out}$ is across the inductor thus,

$$I_L(\text{peak}) = (V_{in} - V_{out}) \frac{t_{ON}}{L}$$

The average current which must match the output current satisfies ,



$$I_L(\text{average at transition}) = \frac{I_L(\text{peak})}{2} = (V_{in} - V_{out}) \frac{dT}{2L}$$

$$= I_{out}(\text{transition})$$

Where, duty ratio, $d = \frac{t_{ON}}{T}$

the output current at the transition point satisfies,
  
$$I_{out}(\text{transition}) = V_{in} \frac{(1-d)d}{2L} T$$



Buck Converter

Discontinuous Mode

➤ Transistor OFF time divided into :

- ❑ segments of diode conduction $d_d T$ and
- ❑ zero conduction $d_o T$.

➤ The inductor average voltage gives ,

$$(V_{in} - V_o)dT + (-V_o)\delta_d T = 0$$

$$\frac{V_{out}}{V_{in}} = \frac{d}{d + \delta_d} \quad --(1)$$

➤ To resolve the value of consider the output current,

$$I_{out} = \frac{I_L(\text{peak})}{2} d + \delta_d$$

➤ the change of current during the diode conduction time ,



$$I_L(\text{peak}) = \frac{V_o(\delta_d T)}{L}$$

Thus, from above equation

$$I_{out} = \frac{V_o \delta_d T (d + \delta_d)}{2L}$$

using the relationship in (1) ,
  
$$I_{out} = \frac{V_{in} d \delta_d T}{2L}$$



Buck Converter

Discontinuous Mode

➤ Solving for the diode conduction ,

$$\delta_d = \frac{2L I_{out}}{V_{in} d T}$$

➤ The output voltage is thus given as ,

$$\frac{V_{out}}{V_{in}} = \frac{d^2}{d^2 + \left(\frac{2L I_{out}}{V_{in} T}\right)}$$

➤ defining $k^* = 2L/(V_{in} T)$,

➤ Output voltage vs. Current

- ❑ High O/p current → voltage ratio depends on the duty ratio "d".
- ❑ Low currents → discontinuous operation tends to increase o/p voltage of the converter towards V_{in} .

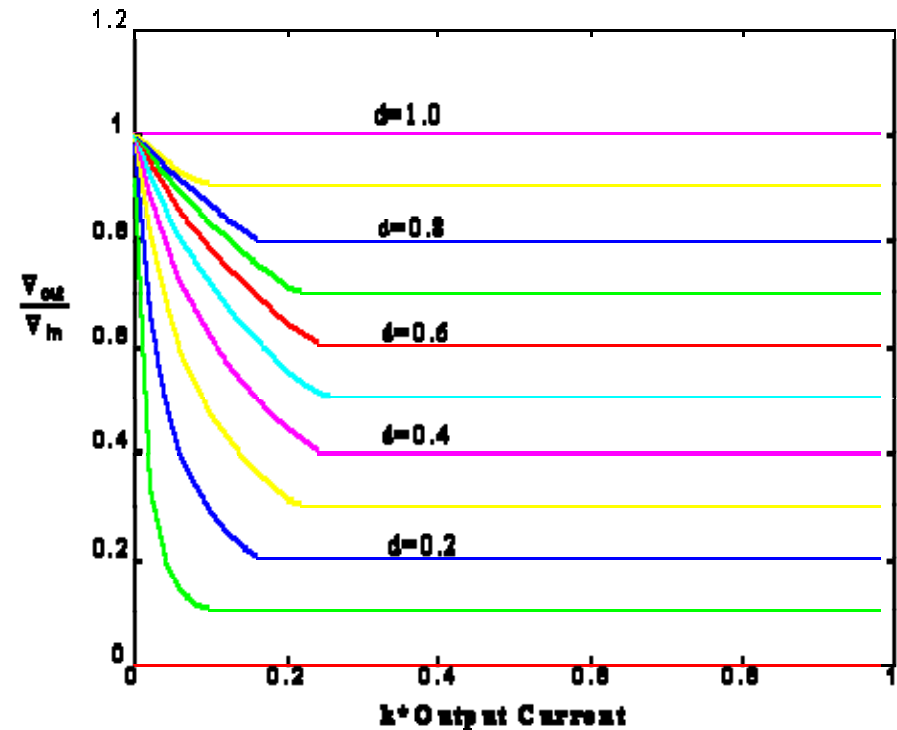
 


Fig. Output Voltage vs Current

Boost Converter

➤ When Transistor "ON"

- $V_x = 0$

➤ When Transistor "OFF"

- $V_x = V_o$

➤ For Steady State

- Voltage across the inductor & average must be zero for the average current.

$$V_{in} t_{on} + (V_{in} - V_o) t_{off} = 0$$

- This can be rearranged to give,

$$\frac{V_o}{V_{in}} = \frac{T}{t_{off}} = \frac{1}{(1-D)}$$

- Since, the duty ratio "D" is b/w 0 and 1 → The output voltage must always be higher than the input voltage in magnitude.

 


Fig. Boost Converter Circuit.

Buck-Boost converter

➤ When Transistor "ON"

- $V_x = V_{in}$

➤ When Transistor "OFF"

- $V_x = V_o$

➤ For Steady State

- Voltage across the inductor & average must be zero for the average current.

$$V_{in} t_{ON} + V_o t_{OFF} = 0$$

- This can be arranged to give voltage ratio as,

$$\frac{V_o}{V_{in}} = -\frac{D}{(1-D)}$$

- Since, the duty ratio "D" is between 0 and 1 → The output voltage may be higher or lower than the input voltage in magnitude.

 


Fig. Buck-Boost Converter Circuit.

Comparison Of Different Converters

- only the buck converter shows a linear relationship.
- The buck-boost can reduce or increase the voltage ratio with unit gain for a duty ratio of 50%.

➤ Buck converter: $\frac{V_o}{V_{in}} = \frac{t_{on}}{T}$

➤ Boost Converter: $\frac{V_o}{V_{in}} = \frac{T}{t_{off}} = \frac{1}{(1-D)}$

➤ Buck-Boost Converter: $\frac{V_o}{V_{in}} = -\frac{D}{(1-D)}$

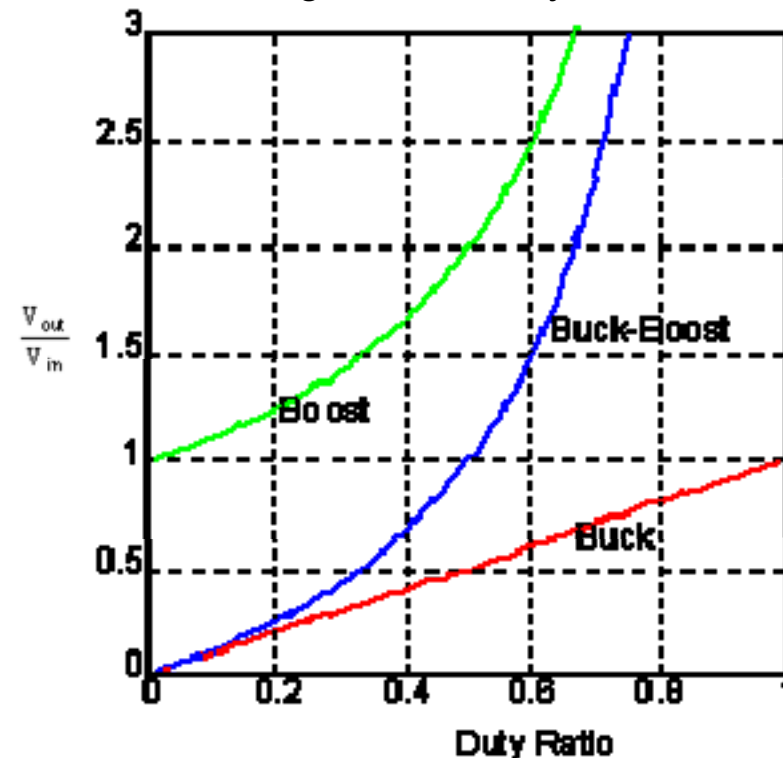


Fig. Comparison Of Voltage Ratio.

Monolithic Integrated DC/DC Converters

Why Monolithic DC/DC Converter?

- Required for portable devices-laptops, mobiles etc.
- Decrease the size & weight of these devices.
- Miniaturization of the power modules.
- Integrating a DC-DC converter can potentially lower the parasitic losses as interconnect b/w DC-DC converter & microprocessor is reduced.
- ❑ Need for on chip, point-of-load (PoL) power conversion.

Challenges

- Tight area constraint for the on-chip integration of inductive & capacitive elements.
- Poor parasitic impedance characteristics.
- High frequency → low value & physical size of passive devices required.

Monolithic Integrated DC/DC Converters

Applications

- Battery operated portable electronic devices like Laptops, cell phones, PDAs (Personal digital assistants) & other palm devices.

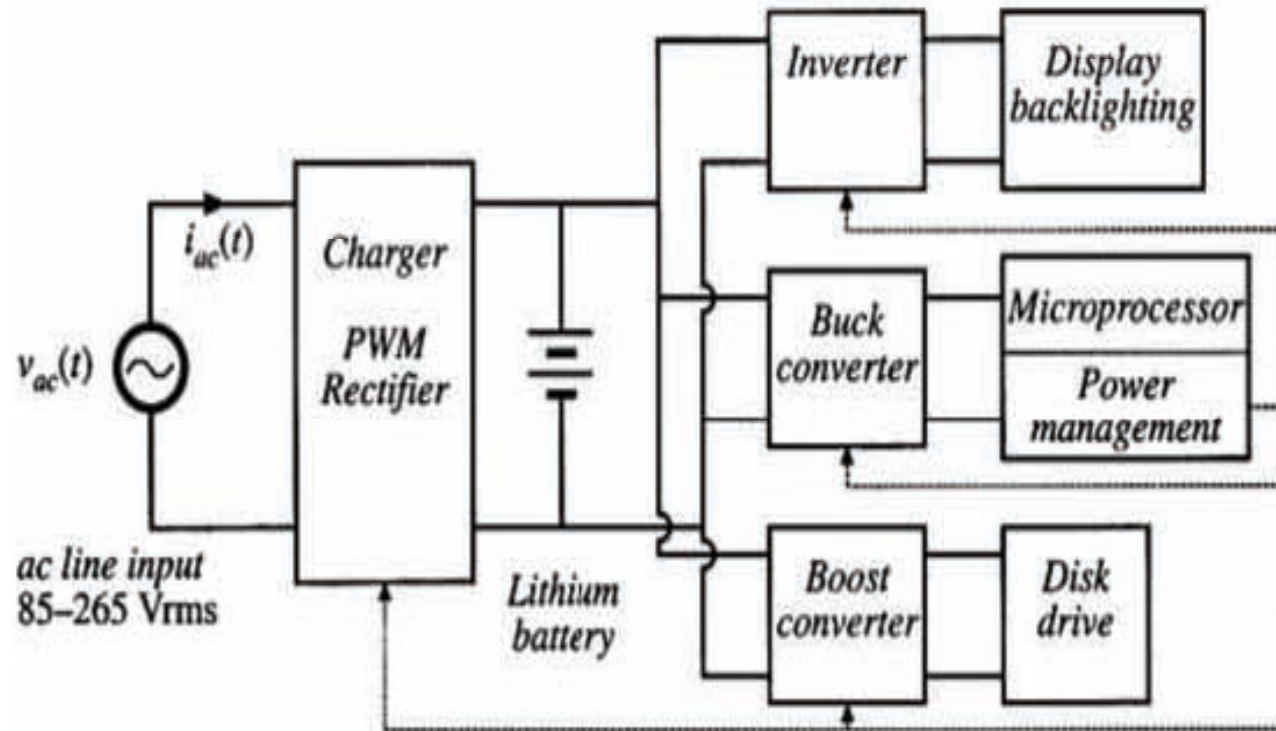


Fig. Laptop Computer power supply system.

Monolithic Integrated DC/DC Converters

Components

- Power Stage
- Compensator
- Modulator
- Voltage to current converter
 - ▣ Sensed Inductor Signal
 - ▣ Ramp signal
- Oscillator & ramp generator
- Pulse width generator
- Buffer

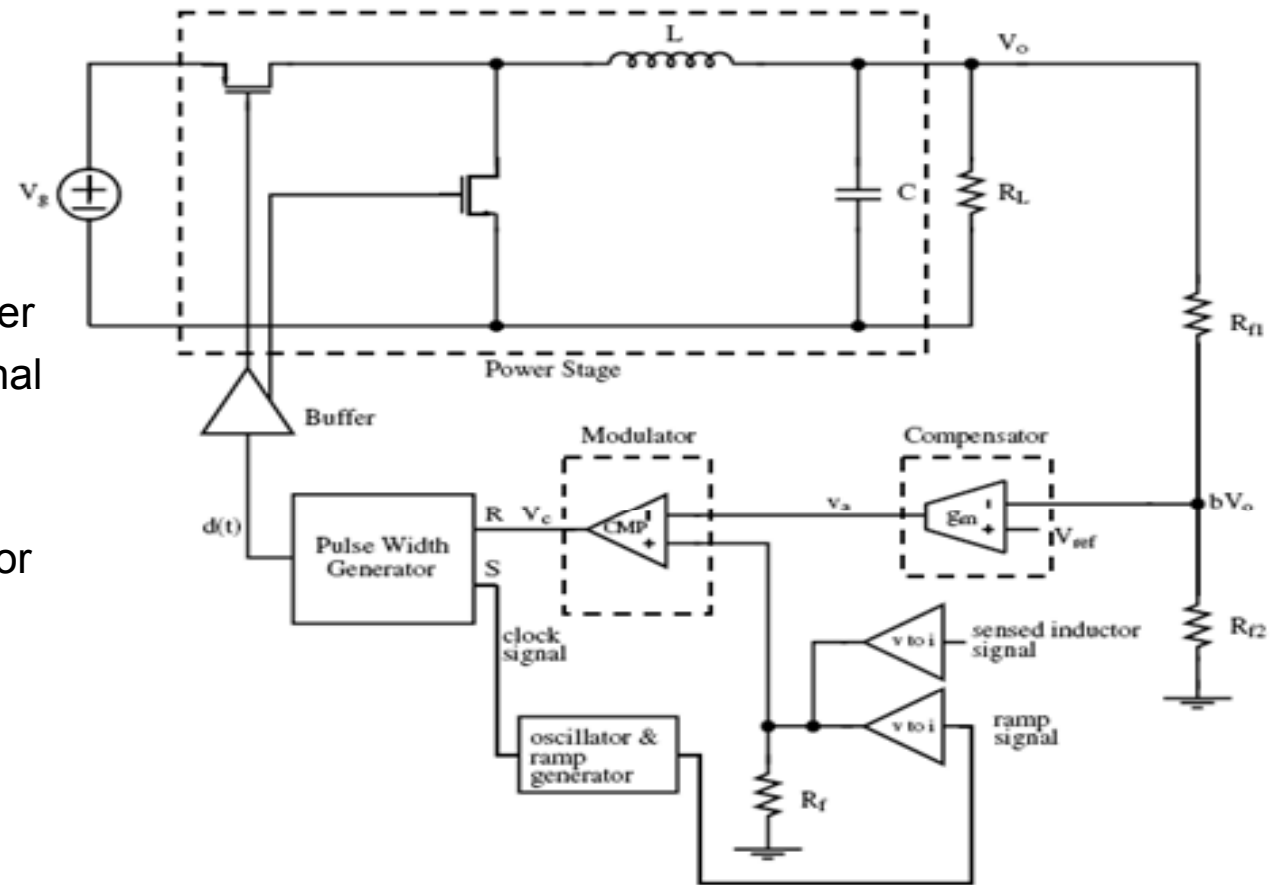


Fig. Structure of a Current Mode Buck Converter.

Power stage: Inductors for On Chip DC/DC Converter (MHz Frequency)

- MEMS based inductors.
- Use iron-based alloy plated on Si substrate.
- Is a metal slab completely encapsulated by a magnetic material.
- Spirals made of $1\mu\text{m}$ Al-Cu isolated from ground plane by $0.5\mu\text{m}$ of SiO_2 .
- The magnetic film surrounding metal is amorphous CoZrTa alloy that exhibits:-
 - ❑ small hysteresis losses.
 - ❑ Withstand temperature up to 450°C .
 - ❑ Integrated in standard high temperature CMOS Si process.
 - ❑ Cut off frequency of approx. 1.4GHz.
- Superior higher frequency & saturation characteristics.
- Reduces size & parasitic effects.
- Performs at frequency up to & beyond 10 MHz.
- Magnetic material below & above spirals prevent straying of magnetic flux.
- One layer of magnetic material increases inductance by 36-50% & two layers by 100-500%.

 


Fig. Schematic of Thin File Inductor.

Power stage: Inductors for On Chip DC/DC Converter (MHz Frequency)

- CoHfTaPd – Co based amorphous alloy can also be used at high frequency (few MHz) .
 upper magnetic layer (CoHfTaPd) coil conductor (copper)

 
 


Fig. Circuit model of single layer spiral circuit.

 


Fig. Top view of monolithic DC-DC converter. Size of inductor (4mm* 4mm)

TOWARDS HIGHLY EFFICIENT MONOLITHIC DC/DC CONVERTER

Power Stage:Capacitors for On Chip DC/DC Converter (MHz frequency)

- Limited area overhead → Filter Capacitance integrated on a Microprocessor die is limited.
- Ranges between 100nF – 1nF.
- As Capacitance (↓) → Filter inductance & switching frequency both increased to satisfy o/p voltage & current.
 - Switching & Conduction power dissipation of power MOSFETS & filter inductor(↑) .
 - Efficiency degrades (↓).

Compensator

Cascode OTA (Operational Trans-conductance Amplifier)

for Power Stage of current mode converter

- ❑ Control-to-o/p transfer function has real poles
- ❑ Pole from o/p filtering capacitor heavily dependent on equivalent resistance of load R_L .
- ❑ Poor frequency response.

➤ **Dynamic Response** → **Pole-Zero Cancellation Preferred.**

- ❑ Band width can be extended.
- ❑ Speed up Response time

$$\text{Tr } A(s) = \frac{V_a}{bV_o} \approx g_m R_o \frac{1 + sC_c R_z}{1 + sC_c R_o}$$

→

, for $R_o \gg R_z$.

where, g_m → Trans-conductance of OTA
 R_o → O/p resistance of the OTA.

 


Fig. Schematic of Pole-Zero cancellation Compensator.

Compensator


- g_m & R_o → important for frequency compensation
- determine gain & phase margin of DC/DC converter
- depend on biasing current

Result

- Average -20 dB/dec closed loop-gain.
- Sufficient phase margin below unity gain frequency.
- Two Stage OTA → Higher gain
 - Large output swing

Cascode OTA (Operational Trans-conductance Amplifier)

Circuit Implementation

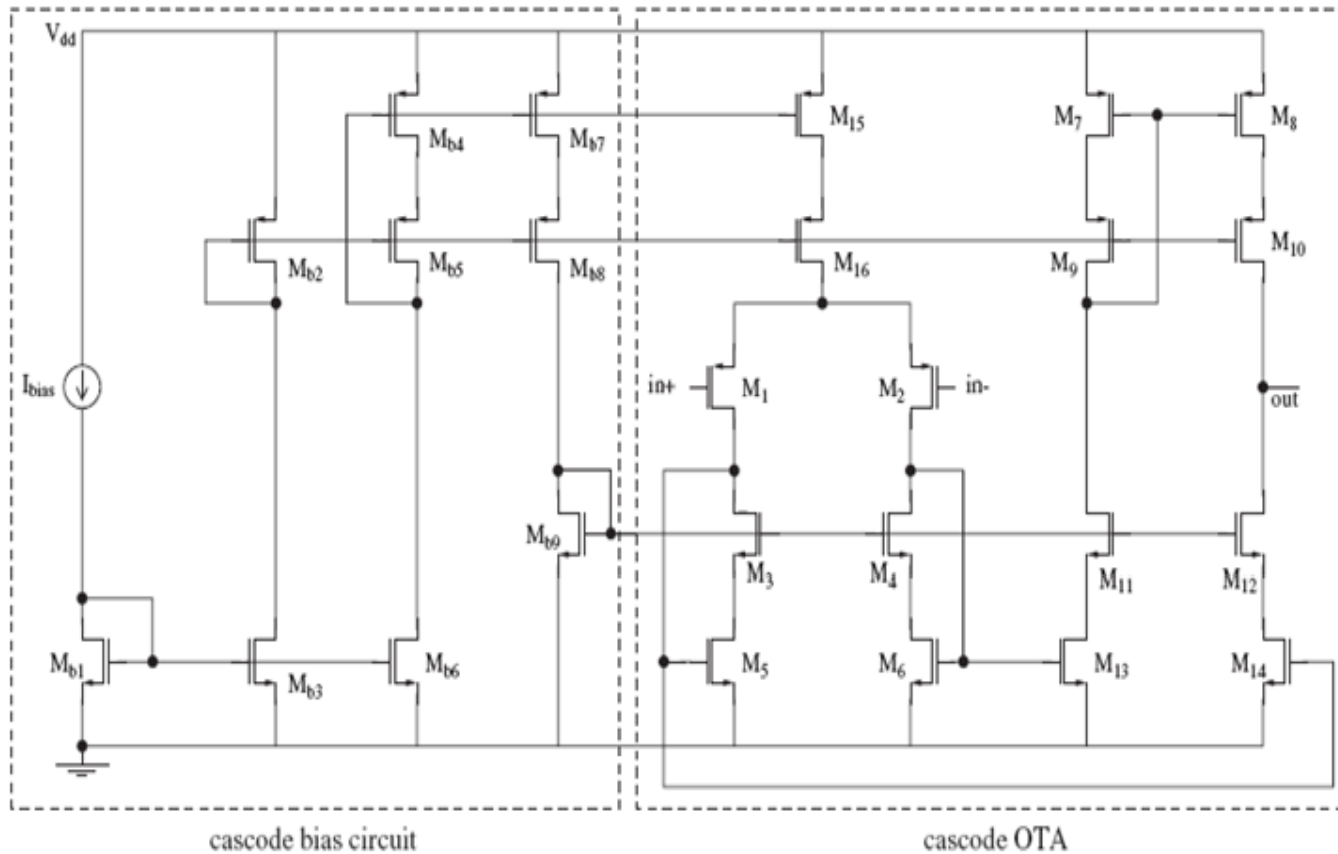

- ✓ Single Stage Amplifier
- ✓ High gain & only one dominant pole

Fig. Schematic of the Cascode OTA.

On Chip Current Sensing Technique (to Sense Inductor Signal)

- Aspect ratio of $M_2 \ll M_1$ in power stage.
- Op amp enforce same voltage at node A & B.
- O/p current I_o flows through M_1 .
- Switch MS_1 is shorted.
- $V_{DS}(M_1) = V_{DS}(M_2)$
- I_s (Sensing current) $\ll I_o$
- $I_2 \ll I_s$
- V_{sense} in control feedback loop
- M_{rs} operate in saturation

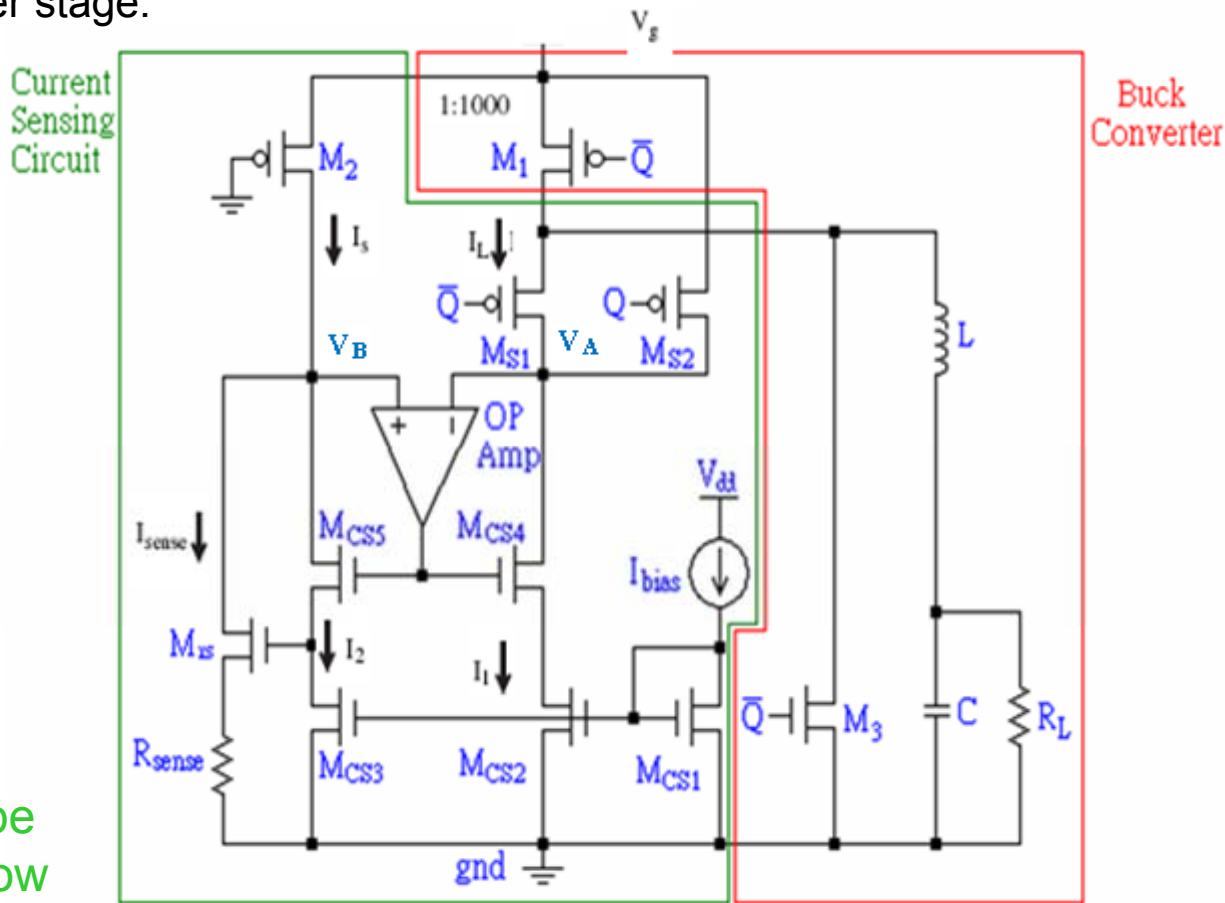


Fig. Schematic of on Chip Current Sensing Circuit.

The sensing scheme needs to be realized with high bandwidth & low power consumption.

On Chip Current Sensing Technique (to Sense Inductor Signal)

Characteristics

- $V_{\text{sense}} = I_{\text{sense}} R_{\text{sense}} = I_L R_{\text{sense}} / 1000$
- High gain amplifier required for accurate current sensing.
- Accuracy of sensed current depend on:
 - ❑ current mirror M_1 & M_2 .
 - ❑ On-chip resistor R_{sense} .
- Matching of M_1 & M_2 depend on:
 - ❑ Mobility, μ
 - ❑ Oxide capacitance, C_{ox} .
 - ❑ Threshold voltage, V_T .
 - ❑ Location of M_2 to minimize error.

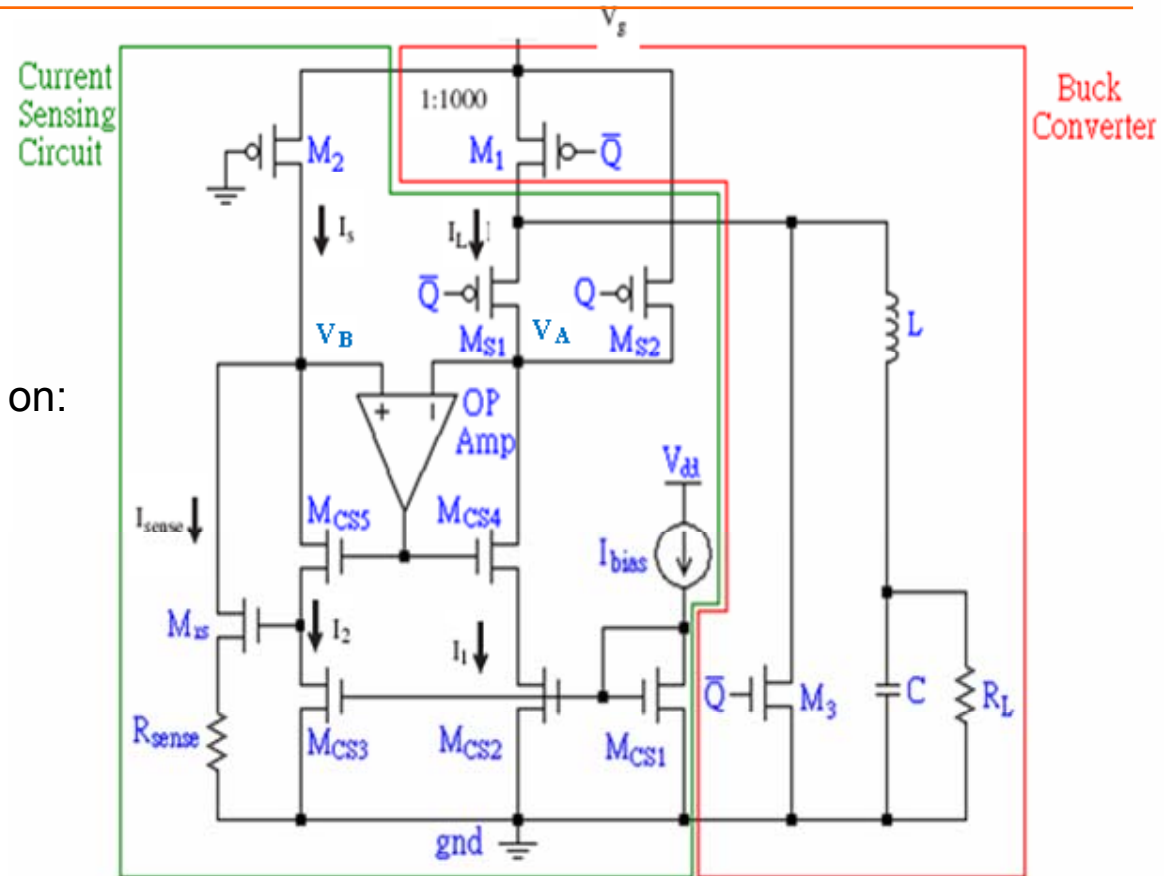


Fig. Schematic of on Chip Current Sensing Circuit.

On Chip Current Sensing Technique (to Sense Inductor Signal)

Advantages

- I_{sense} → small
 - Hence, power loss reduced in the sensing circuit.
 - Improve efficiency of converter.

On-chip current-sensing circuit can be extended to sense power NMOS transistor by building complementary circuit for other topologies – boost converter & buck-boost converter.

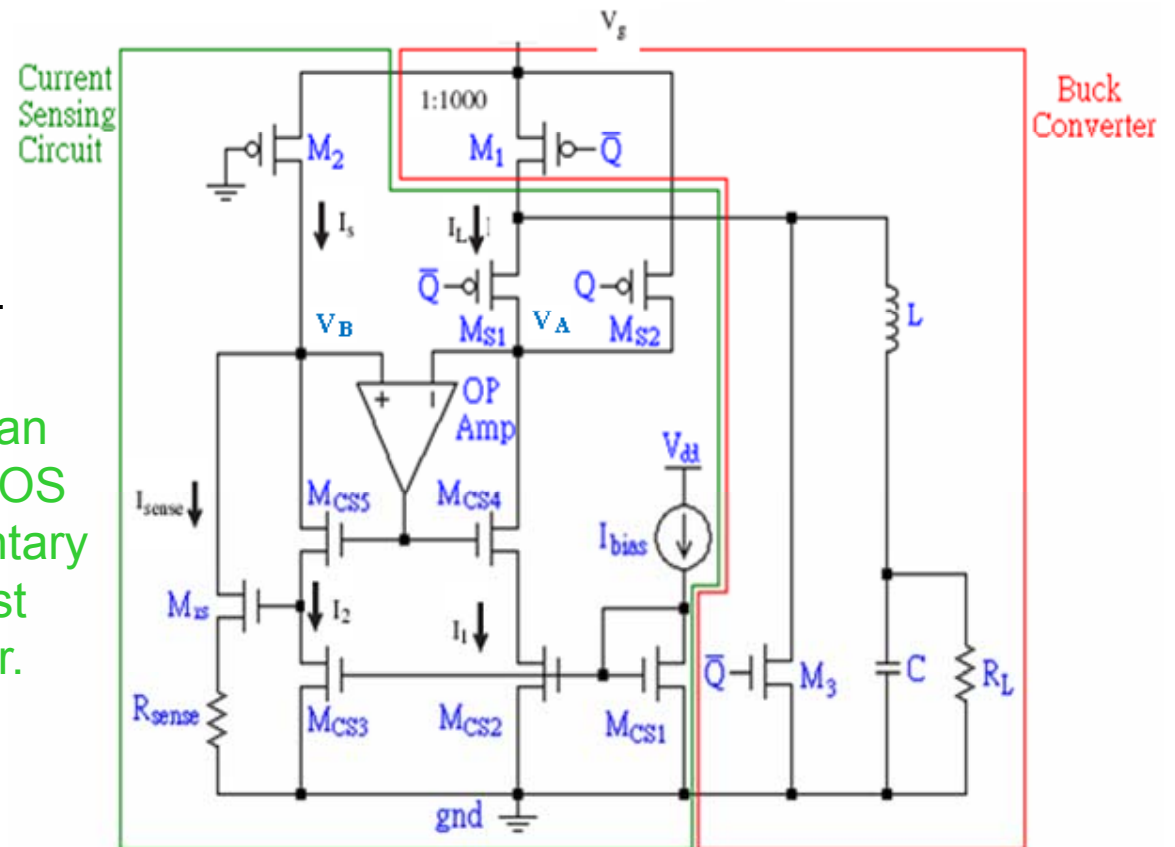


Fig. Schematic of on Chip Current Sensing Circuit.

Modulator (Comparator)

Comparator

- Needed in both:
 - modulator in feedback control (PWM control).
 - hysteretic comparator in the Oscillator & ramp generator circuit.
- Implemented by a source-coupled differential pair with positive feedback to provide a high gain.
- Gain of positive feedback gain stage is:

$$A_p = \frac{\mu_p \left(\frac{W}{L}\right)_1}{\sqrt{\mu_n \left(\frac{W}{L}\right)_2}} \frac{1}{(1 - \alpha)}$$

where, $\alpha = \frac{\left(\frac{W}{L}\right)_5}{\left(\frac{W}{L}\right)_3}$ is the positive feedback factor.

 


Fig. Schematic of the Comparator.

Comparator

Use of Inverter Chains

- Inverter chains M_{12} - M_{15}
- Increase the response of comparator o/p signal.
- Act as driver stage such that:-
 - M_7 & M_8 can be made smaller.
 - Reduce parasitic capacitance at gates of M_7 & M_8 .
 - Results Faster Response.

 


Fig. Schematic of the Comparator.

Simulation: 15ns delay time → Adequate for applications with switching frequency of few MHz.

Oscillator and Ramp Generator

➤ Used to generate:

- ❑ the clock & ramp signals for PWM control.
- ❑ Compensation slope for current mode converter

➤ Consists of:

- ❑ Voltage-to-current(V-I) converter.
- ❑ Hysteretic comparator.

➤ Clock frequency & slope of compensation ramp are:

- ❑ Synchronized with each other.
- ❑ Depend on v_{ref} , C_t , R_t , V_H & V_L .

 


Fig. Schematic of the Oscillator and Ramp Generator.

R_t & C_t can be off-chip components → Switching frequency can be adjusted for different applications.

V-I Converter

- In current mode converters, compensation ramp add with inductor current signal to avoid sub harmonic oscillations.
- V-I designed to convert ramp signal & sensing inductor signal into current.
- V-I converter is a cascade of:
 1. Source follower
 2. Common-source config.
 & sensing voltage range from 300-1000mV.
 - ❑ Not high enough to turn 'ON' M_2 & M_4 .

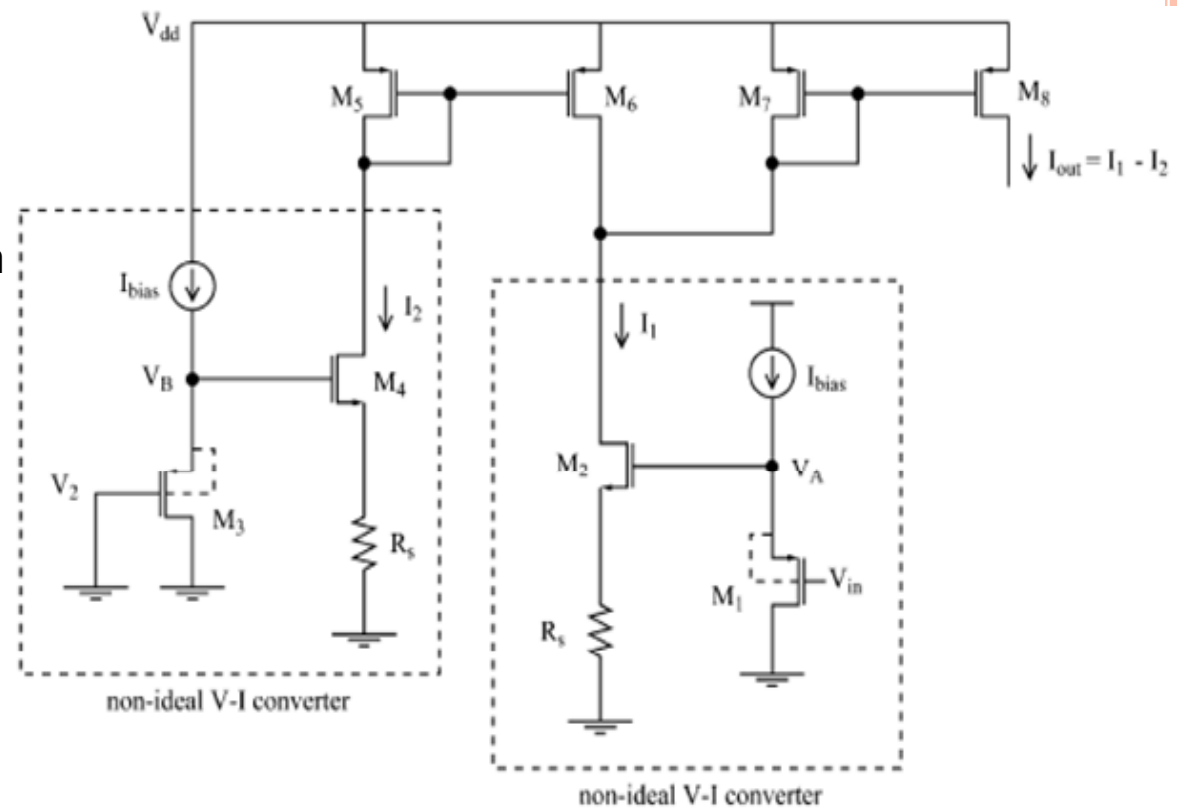


Fig. Schematic of the V – I Converter.

V-I Converter

➤ Now, $V_A = V_{in} + V_{SG1}$

➤ For 2nd stage V-I converter:

Trans-conductance,

$$G_{m2} = \frac{I_1}{V_A} = \frac{g_{m2}}{1 + g_{m2} R_s} \approx \frac{1}{R_s} \text{ for } g_{m2} R_s \gg 1$$

Then, the o/p current is given by,


$$I_1 = \frac{V_A}{R_s} = \frac{V_{tn} + V_{SG1}}{R_s}$$

➤ Need to eliminate non-ideal term, $\frac{V_{SG1}}{R_s}$

➤ Now, $I_2 = \frac{V_{SG3}}{R_s}$

➤ Hence, o/p current I_{out} ,
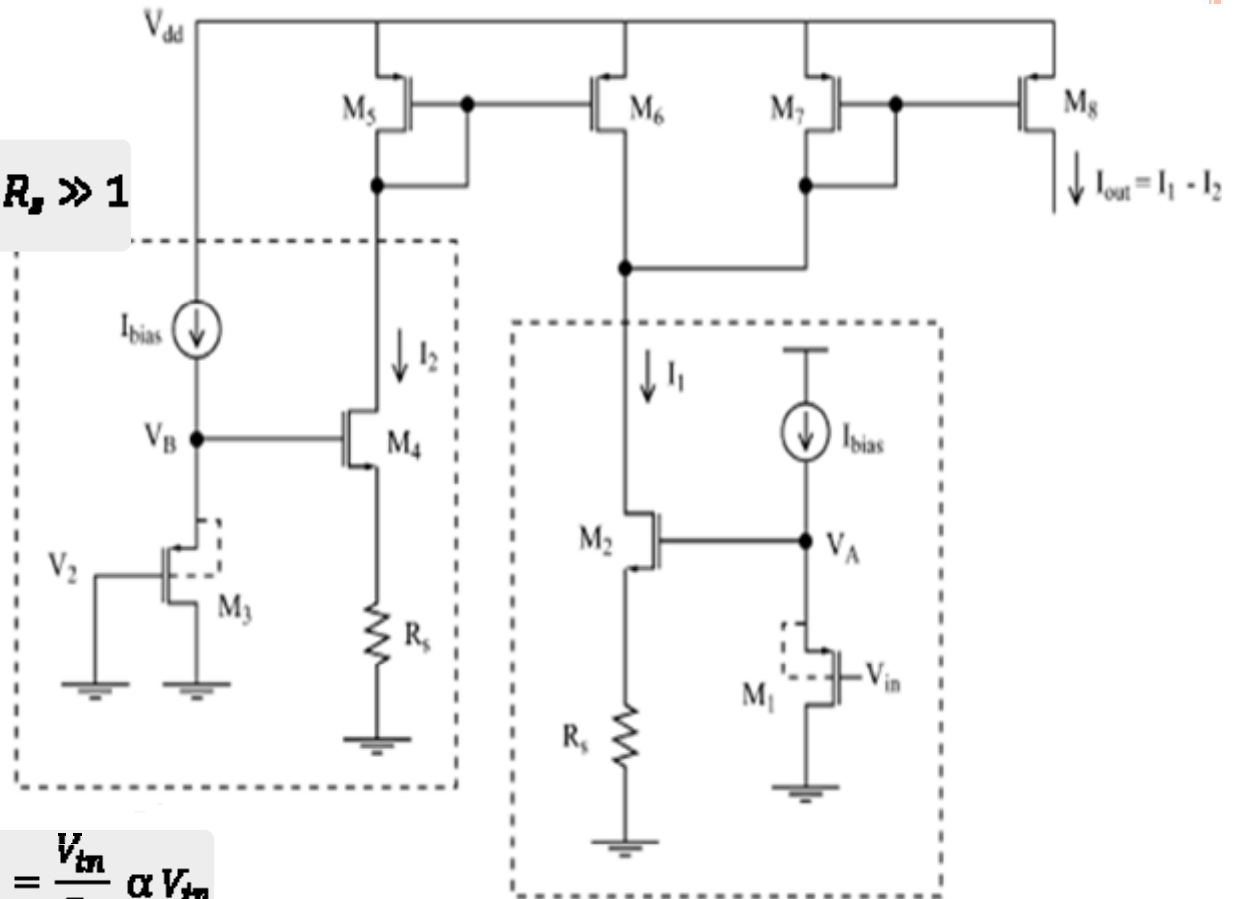
$$I_{out} = I_1 - I_2 = \left(\frac{V_{tn}}{R_s} + \frac{V_{SG3}}{R_s} \right) - \frac{V_{SG1}}{R_s} = \frac{V_{tn}}{R_s} \propto V_{tn}$$



V-I Converter

➤ Now, sensing voltage, $V_{\text{sense}} = I_{\text{sense}} R_{\text{sense}}$

➤ Hence, o/p current, I_{out}

$$I_{\text{out}} = \frac{V_{\text{sense}}}{R_s} = I_{\text{sense}} \left(\frac{R_{\text{sense}}}{R_s} \right)$$

➤ I_{out} & I_{sense} do not depend on value of R_s & R_{sense} , rather on the ratio

▣ Can be easily controlled.

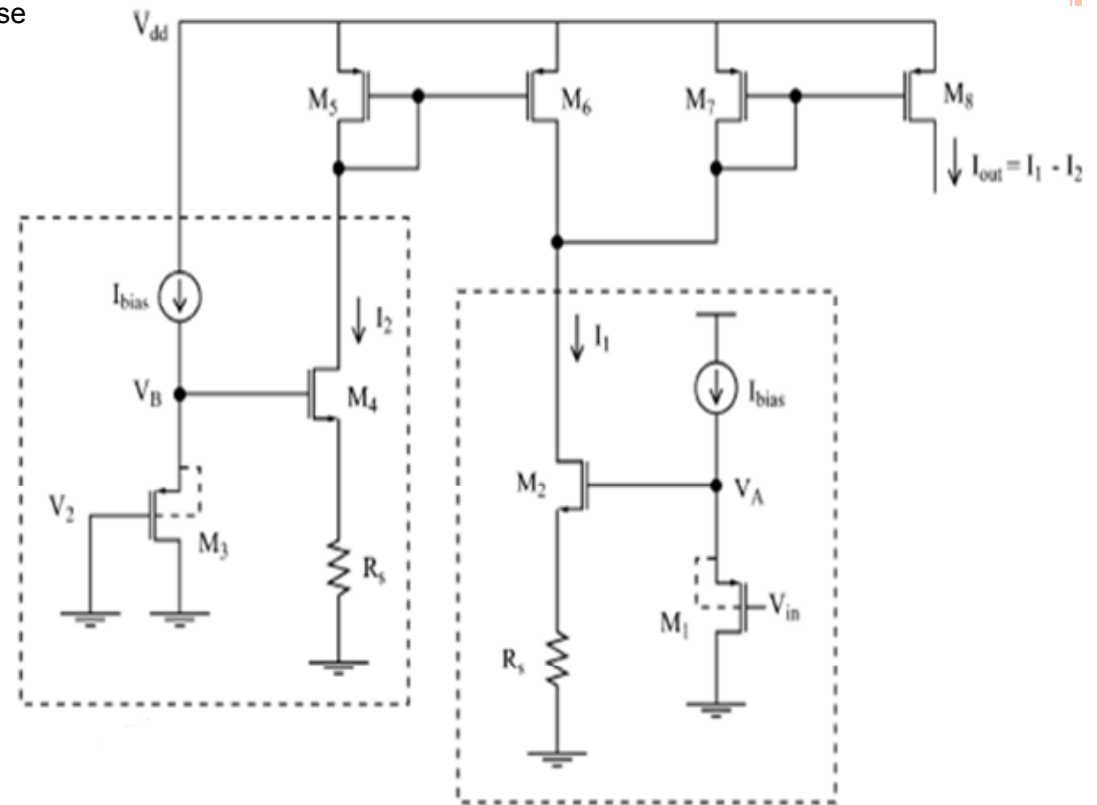


Fig. Schematic of the V – I Converter.

Pulse width Generator

- $S=1, R=1$ is a forbidden state for the SR Latch.
- At startup, O/p of compensator V_c is low compared with sum of the ramp & sensed signal.
- Hence, R is always High.
- However, the given circuit ensures that RS latch do not reach forbidden state.
- R & S do not go High simultaneously.

 


Fig. Schematic of Pulse width Generator.

Buffer

- Required for receiving and amplifying the signal produced by the control circuit.
- Poorly designed buffer with a simple inverter Chain → a shoot-through current will occur and a large current will pass through the power transistors during each switching transition.
- Hence, buffer without short-circuit power consumption is needed.
- Power rails of the buffer should be laid-out carefully & resistances to be minimized So that the converter efficiency do not degrade.

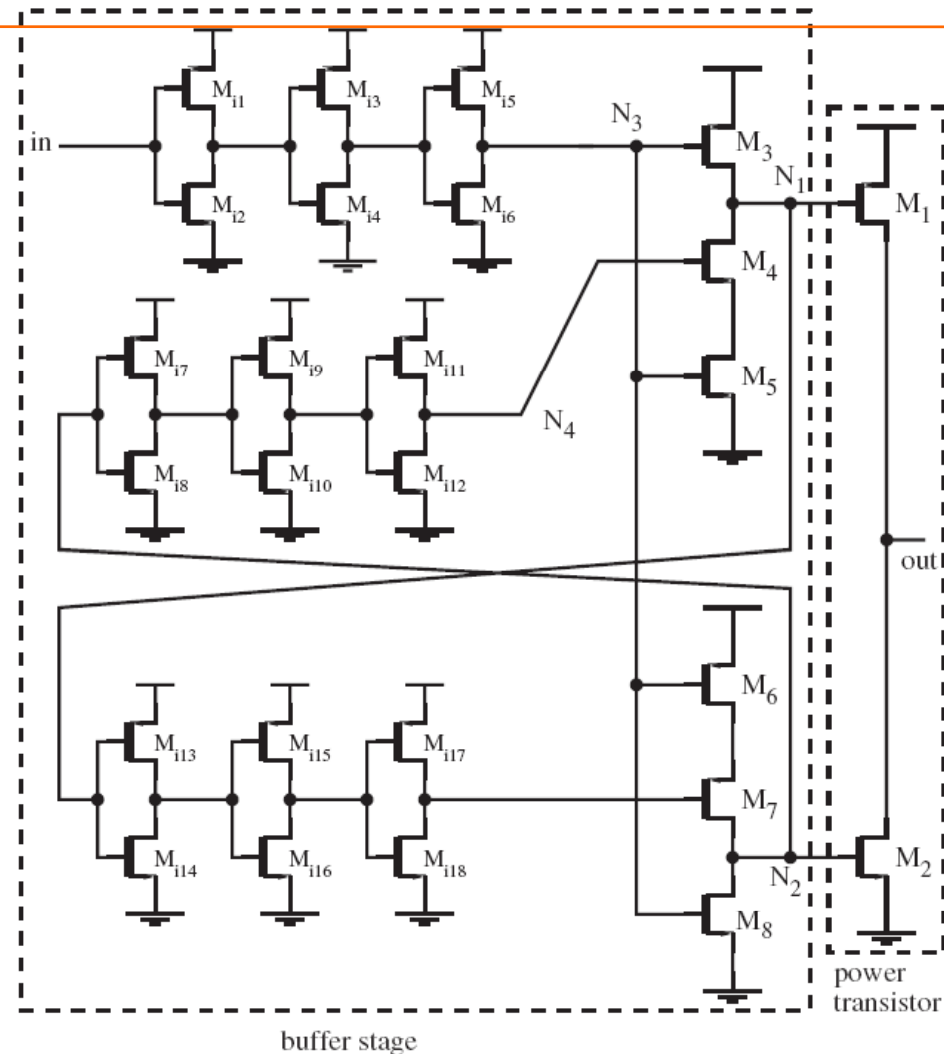


Fig. Schematic of Buffer without short-circuit power consumption.

Power Losses in DC/DC Converter

- **Conduction Loss**
 - **Switching Loss**
- } Related to the size of Power Transistors
□ Optimum Sizing required to improve Efficiency.
- **Shoot through current Loss**
- } Related to design of buffer Stage to drive power transistors.
- Significant energy dissipated in parasitic impedances of circuit board inter connect & discrete components of the regulator.
 - **Conduction Losses:** Caused by the parasitic resistive impedances.
 - **Switching Losses:** Due to parasitic capacitive impedances of circuit components.
 - Power consumed by PWM feedback circuit & integrated filter capacitor is small as compared to the power consumption of the power train (the power MOSFETs, MOSFET gate drivers, the filter inductor).

Power Flow Analysis in DC/DC Converter

- Buck converter O/p, $V_{DD2}(t) = DV_{DD1} + V_{\text{ripple}}(t)$.
- Ripple Current, $\Delta i = (V_{DD1} - V_{DD2})D/2Lf_s$.
- Amplitude of voltage ripple,

$$\Delta V_{DD2} = \frac{(V_{DD1} - V_{DD2})D}{16LCf_s^2} = \frac{\Delta i}{8Cf_s}$$

where, L → Filter inductance.

C → Filter Capacitor.

f_s → Switching frequency.

 


Fig. Inductor Current $i_L(t)$, Output voltage $V_{DD2}(t)$, capacitor current $i_C(t)$ waveforms.

Power Flow Analysis in DC/DC Converter

➤ MOSFETs Related Power

- Combination of Conduction loss & Dynamic Switching loss.
- Conduction power → Dissipated in series resistance of transistor
- Dynamic Power → Dissipated in each switching cycle of charging/discharging of Gate oxide, gate-to-source/drain overlap & drain-to-body junction capacitance of MOSFET.
- MOSFET width optimized to minimize power dissipation.
- Optimized power consumption is:

$$P_{tot,MOS}(opt) = a \sqrt{\left(I^2 + \frac{I^2}{3}\right) f_s}$$

$$a = 2\left(\sqrt{R_{oNMOS}(1-D)E_{NMOS}} + \sqrt{R_{oPMOS}DE_{PMOS}}\right)$$

$$E = 2(C_{ox} + C_{gs} + 2C_{gd} + C_{db})V_{DD}f_s^2$$


Where, R_o → equivalent series resistance of a $1\mu\text{m}$ wide transistor.

C_{ox} → gate oxide capacitance.

C_{gs} → gate-to-source overlap.

C_{gd} → gate-to-drain overlap.

 C_{db} → drain-to-body junction capacitance.



Power Flow Analysis in DC/DC Converter

➤ Filter Inductor Power

- Energy consumption due to:
 - Series resistance of filter inductor.
 - Stray capacitance of filter inductor.
- Total power consumption in inductor is:

$$P_{tot,inductor} = b \left(\frac{I^2}{\Delta l f_B} + \frac{\Delta l}{3 f_B} + \frac{C_{Lo} V_{DD1}^2}{R_{Lo} \Delta l} \right)$$

$$b = \frac{(V_{DD1} - V_{DD2}) D R_{Lo}}{2}$$

Where, C_{Lo} ➔ Parasitic stray capacitance per nH Inductance.
 R_{Lo} ➔ Parasitic Series Resistance per nH Inductance.

Power Flow Analysis in DC/DC Converter

➤ Filter Capacitor Related Power

- Integrated Capacitor implemented utilizing Gate Oxide Capacitance of MOSFET
- Total Power dissipation of a filter Capacitor is:

$$P_{tot, capacitor} = d f_s \Delta I$$

$$d = \frac{8R_{ocap} L_{cap} C_o \Delta V_{DD2}}{3}$$

Where, R_{ocap} → Series Capacitance of MOSFET with $1\mu\text{m}$ width.
 C_o → Gate Oxide Capacitance per μm^2 .
 L_{cap} → Channel Length of the MOSFET.

Power Flow Analysis in DC/DC Converter

➤ Total Power Consumption of Buck Converter

$$P_{buck} = P_{tot,MOS} (opt) + P_{tot,inductor} + P_{tot,capacitor}$$

$$P_{buck} = a \sqrt{\left(I^2 + \frac{i^2}{3}\right) f_s} + b \left(\frac{I^2}{\Delta i f_s} + \frac{\Delta i}{3 f_s} + \frac{C_{Lo} V_{DD1}^2}{R_{Lo} \Delta i} \right) + d f_s \Delta i$$

➤ Strongly function of Switching frequency (f_s) & Ripple Current (Δi).

➤ $P_{tot, capacitor}$ (↑) → As f_s & Δi (↑).

➤ $P_{tot, inductor}$ (↓) → As f_s & Δi (↑).

➤ $P_{tot, capacitor}$ → Negligibly small (less than 1%) as compared to Inductor & MOSFET Power.

Efficiency Analysis in DC/DC Converter

Efficiency, η

$$\eta = 100 * \frac{P_{Load}}{P_{Load} + P_{buck}}$$

$$P_{buck} = a \sqrt{\left(I^2 + \frac{l^2}{3}\right) f_s} + b \left(\frac{I^2}{\Delta l f_s} + \frac{\Delta l}{3 f_s} + \frac{C_{Lo} V_{DD1}^2}{R_{Lo} \Delta l} \right) + d f_s \Delta l$$

- Low f_s & Δi \rightarrow Power dissipation mainly in the Inductor.
- As f_s & Δi (\uparrow) \rightarrow Inductor Loss (\downarrow) (Parasitic Loss \downarrow)
MOSFET Power Loss (\uparrow)
- As Inductor loss dominate \rightarrow Loss (\downarrow)

 


Fig. Converter Efficiency as functions of Δi & f_s .

Fig. (a) MOSFET Power (b) Inductor Power (c) Capacitor Power as functions of Δi & f_s .

Δi in Amps & f_s in MHz .

Efficiency Analysis

- As the filter capacitance (↓) → The filter inductance & switching frequency are both (↑) to satisfy the output voltage and current requirements.
- Both the switching and conduction power dissipation of the power MOSFETs and the filter inductor increases.
 - thereby degrading the efficiency.

Major challenges for a monolithic switching DC-DC converter

- The area occupied by the integrated filter capacitor.
- The effect of the parasitic impedance characteristics of the integrated inductors on the overall efficiency characteristics of a switching DC-DC converter.

Light Load Efficiency in DC/DC Converter (to Improve Efficiency)

- Battery-powered portable electronic devices like cell phones, Laptops etc.
- Full loading not present for prolonged periods.
- Rather devices run at light loads (Stand-By mode) for most of the time.

➤ Region I

- Conduction Losses dominate.

➤ Region II

- Switching Losses proportional to load Current, i/p voltage, switching frequency.

➤ Region III

- Gate-drive losses while charging/discharging Gate Capacitances of Power transistors during Switching transition.

 


Fig. Efficiency Curve of DC/DC Converter.


Decreasing Switching Frequency → Best way to Reduce Total Loss.

Compensated Error Amplifier (for Fast Transient Response)

- Fast transient response of o/p voltage reveals critical point for large load variations.
- Required to supply reliable voltage.

Solution

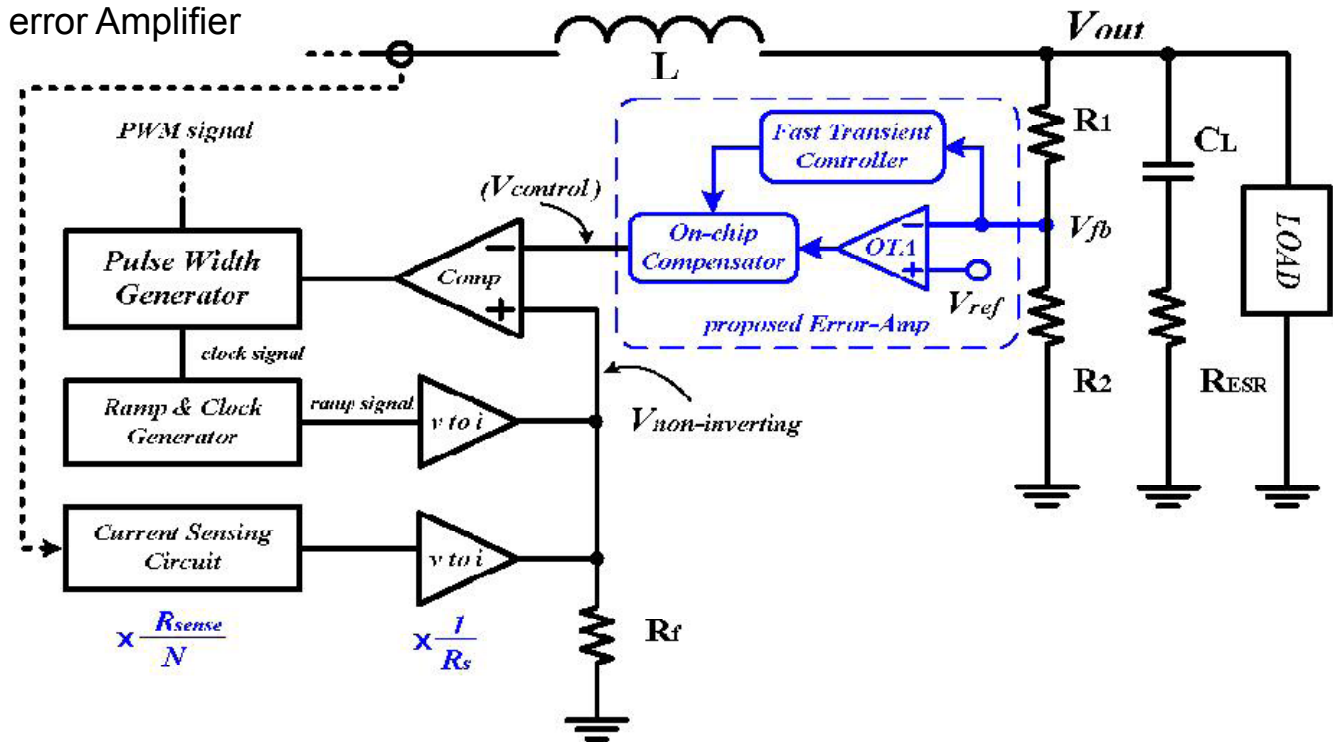- Large Transconductance for the error Amplifier For large load variations.
- Uses on-chip current mode Miller capacitor (replaces large Off capacitor).
- Decrease transient response Time.



Compensated Error Amplifier (for Fast Transient Response)

 


Fig. Timing Analysis of signal waveforms. (a) With a positive & sudden load variation. (b) With a negative & sudden load current variation.

Compensated Error Amplifier (for Fast Transient Response)

- Better Response Time.

 


Fig. The transient response with load current step b/w 100mA & 400mA. (a) Conventional error amplifier. (b) On-chip compensated error amplifier without fast transient controller. (c) On-chip compensated error amplifier with fast transient controller.

Issues with Monolithic DC/DC Converters

- High Efficiency with large input voltage range.
- High Performance System-on-chip (SOC) systems
- Dynamic Power Management
- Fast Dynamic Response
- Low Power Consumption: low stand by power.
- Need to provide robust Output Voltage regulation
- Maximum Efficiency
- Minimize Ripple noise on Input & Output
- Minimize cost
- To have accurate sensed current for current mode PWM controller
- Reduce supply voltage demand, greater amount of current from external power supplies .
- Voltage scaling capability.

References

Books

- R.W. Erickson, “*Fundamentals of Power electronics*”; Kluwer academic Publications, N.J. USA, 2nd Edition, 2001.

Research Papers

1. C.F. Lee, P.K.T Mok; “A Monolithic Current-Mode CMOS DC–DC Converter With On-Chip Current-Sensing Technique”, IEEE journal of Solid-State circuits, vol. 39, issue-1, Jan. 2004, pp. 3-14.
2. V. Kursun, S.G. Narendra, V.K. De, E.G. Friedman; “Low-Voltage-Swing Monolithic dc–dc Conversion”, IEEE transactions on circuits and systems, vol. 51, issue 5, May 2004, pp. 241-248.
3. V. Kursun, S.G. Narendra, V.K. De, E.G. Friedman; “Analysis of Buck Converters for On-Chip Integration With a Dual Supply Voltage Microprocessor”, IEEE transactions on VLSI systems, vol. 11, issue 3, June 2003, pp. 514-522.
4. Y. Katayama, S. Sugahara, H. Nakazawa, M. Edo; “High-Power-Density MHz Switching Monolithic DC-DC Converter with Thin-Film Inductor”, IEEE 31st Annual Power Electronics Specialists Conference 2000, vol. 3, 18th-23rd June 2000, pp. 1485-1490.
5. S. Zhou, G.A.R. Mora; “A High Efficiency, Soft Switching DC–DC Converter With Adaptive Current-Ripple Control for Portable Applications”, IEEE transactions on circuits and systems, vol. 53, issue 4, April 2006, pp. 319-323.
6. H.W. Huang, H.H. Ho, C.C. Chien, K.H. chen, G.K. Ma, S.Y. Kyo; “Fast Transient DC-DC Converter with On-Chip Compensated Error Amplifier”, Proceedings of the 32nd European solid-State Circuits Conference 2006, sept. 2006, pp. 324-327.

Questions???

THANK YOU !!!