

CMOS Thyristor Based Low Frequency Ring Oscillator

Presented By: Piyush Keshri (Y5303)
Biplab Deka (Y5147)

Mentor: Prof. S. Qureshi

Outline

- ❑ Overview of Ring Oscillators
- ❑ Simple Inverter Chain
- ❑ Current Starved Inverter Chain
- ❑ CMOS Thyristor Based Inverter
- ❑ CMOS Thyristor with Footer
- ❑ Comparison
 - ❑ Voltage Sensitivity
 - ❑ Temperature Sensitivity
- ❑ References

Outline

- ❑ Overview of Ring Oscillators
 - ❑ Simple Inverter Chain
 - ❑ Current Starved Inverter Chain
 - ❑ CMOS Thyristor Based Inverter
 - ❑ CMOS Thyristor with Footer
- ❑ Comparison
 - ❑ Voltage Sensitivity
 - ❑ Temperature Sensitivity
- ❑ References


Overview of Ring Oscillators

- **Design of Ring Oscillators**
 - Typically odd number of inverters
 - Used as delay cells
 - connected in cascade & in a closed loop
- **Oscillation frequency given by:**

$$f = \frac{1}{2N\tau_d}$$

Where, $N \rightarrow$ is the No. of delay cells.

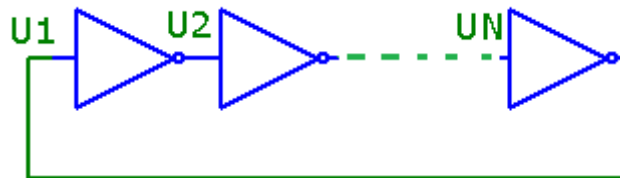$\tau_d \rightarrow$ is the delay time in each cell.





AIM: Design Oscillator with Frequency = 1 kHz.
V_{dd} = 1.2 volts.


Outline

- ❑ Overview of Ring Oscillators
- ❑ Simple Inverter Chain
- ❑ Current Starved Inverter Chain
- ❑ CMOS Thyristor Based Inverter
- ❑ CMOS Thyristor with Footer
- ❑ Comparison
 - ❑ Voltage Sensitivity
 - ❑ Temperature Sensitivity
- ❑ References


Simple Inverter Chain

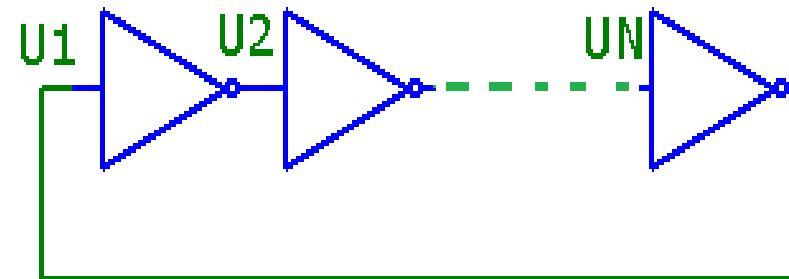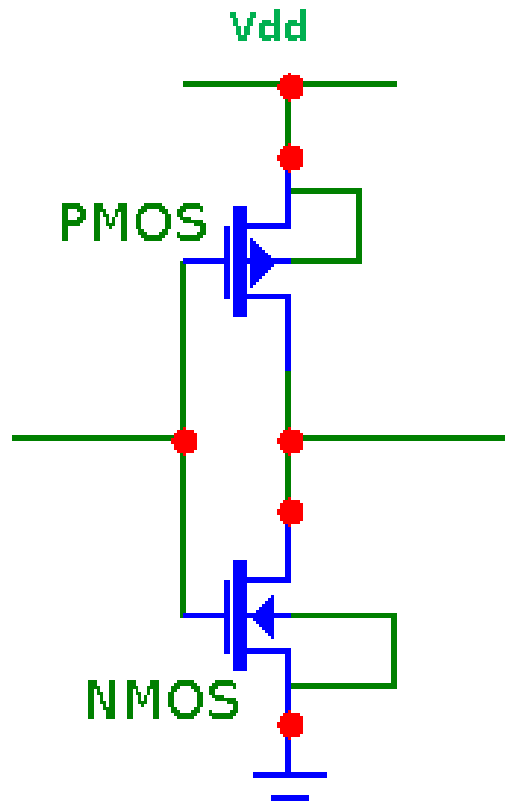

Simple Inverter Chain

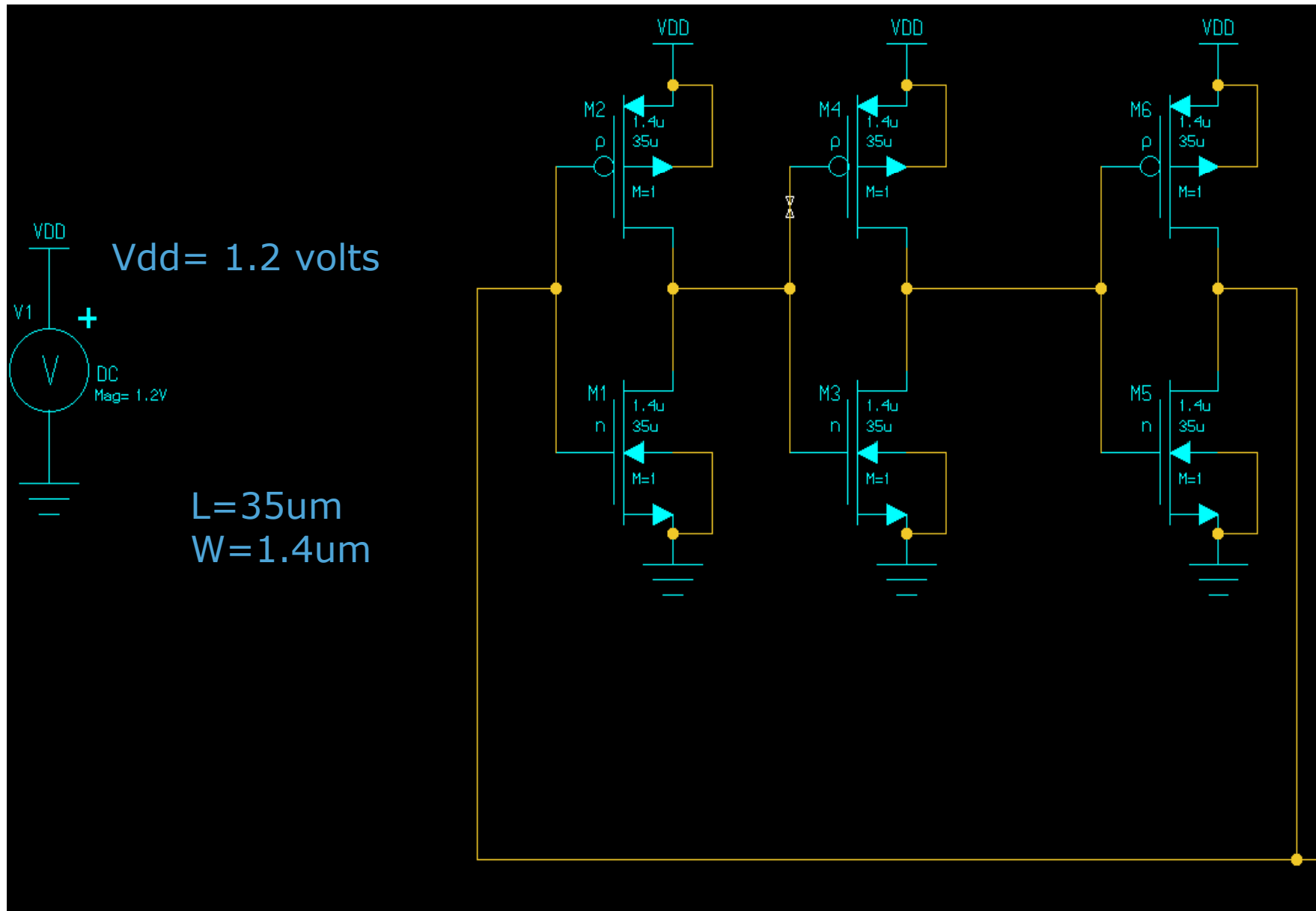

Simple Inverter Chain

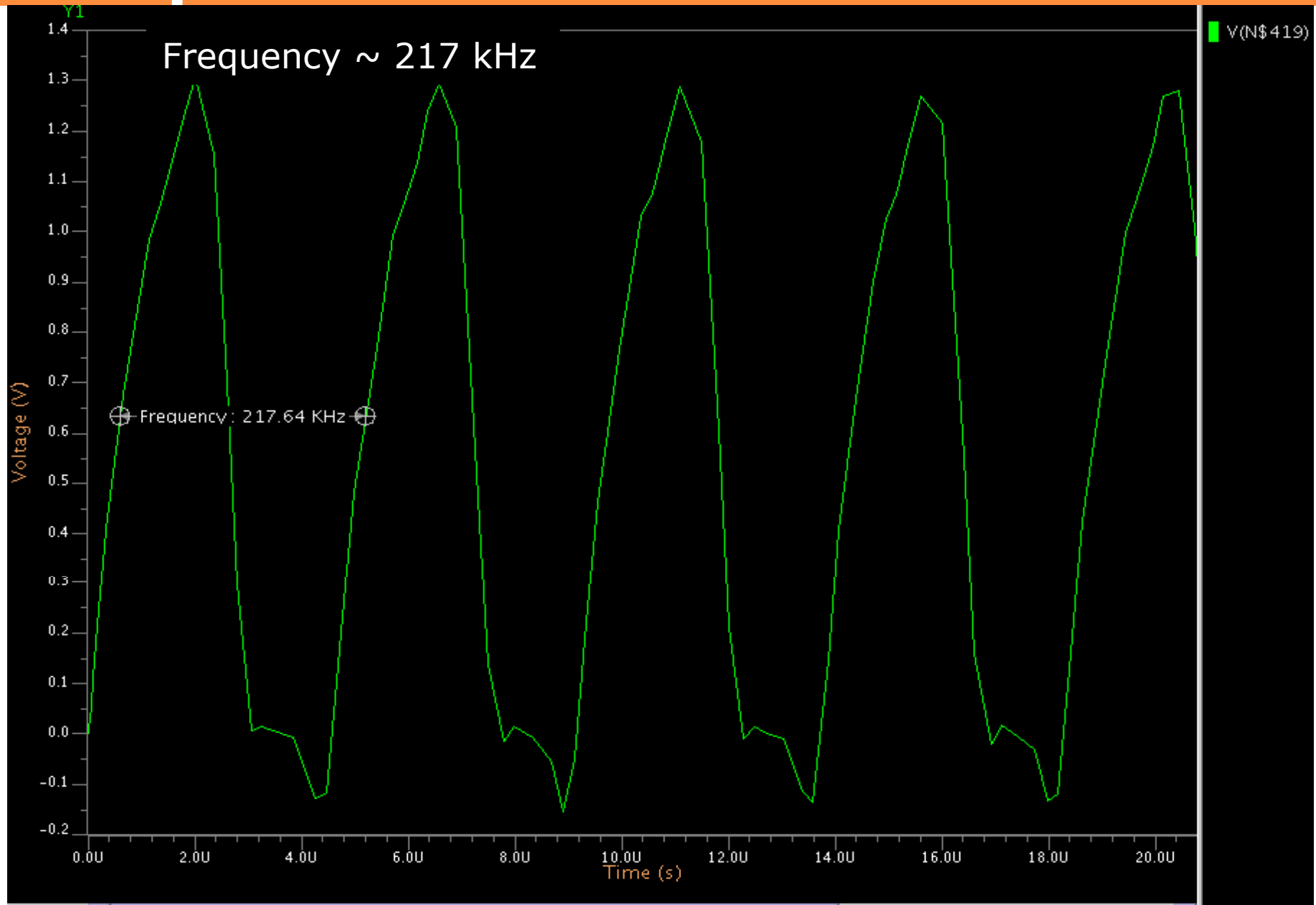


Simple Inverter Chain

- **To Achieve Frequency = 1 kHz**
 - No. of Inverters = 601
 - $L = 35\mu\text{m}$
 - $W = 1.4\mu\text{m}$
 - **Power Consumption = 716 nW**

Outline

- ❑ Overview of Ring Oscillators
- ❑ Simple Inverter Chain
- ❑ **Current Starved Inverter Chain**
- ❑ CMOS Thyristor Based Inverter
- ❑ CMOS Thyristor with Footer
- ❑ Comparison
 - ❑ Voltage Sensitivity
 - ❑ Temperature Sensitivity
- ❑ References


Current Starved Inverter Chain

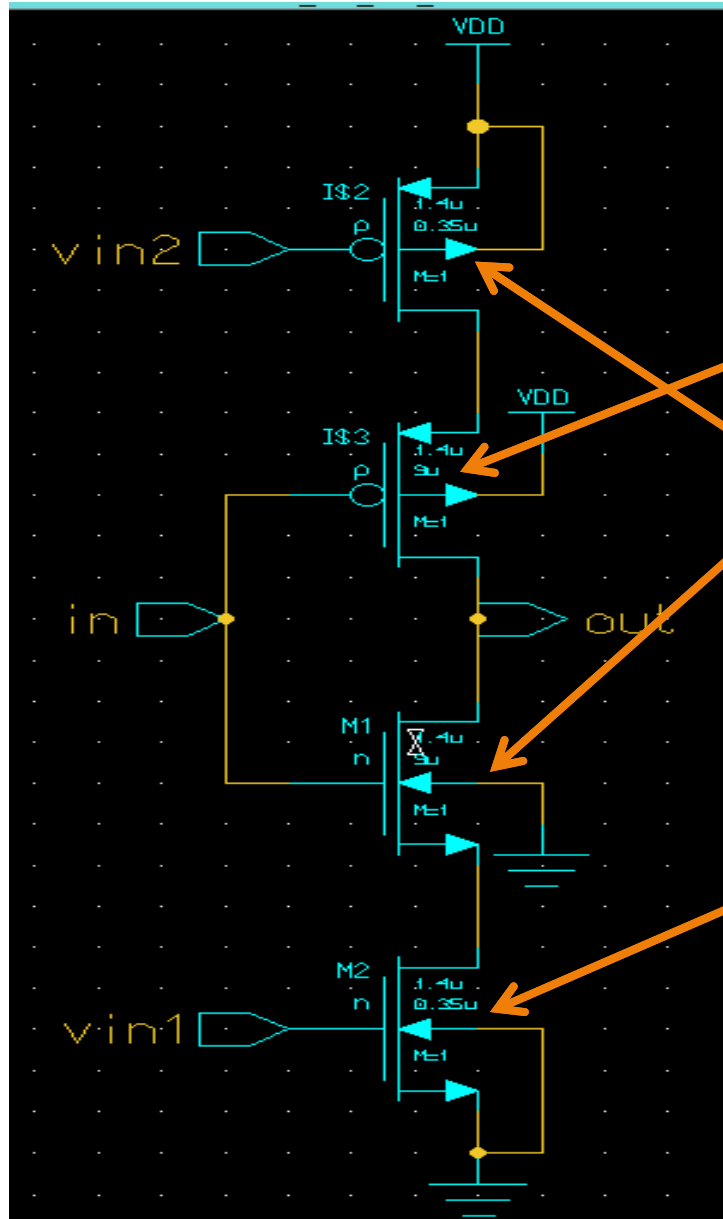


L=9um
W=1.4um

L=0.35um
W=1.4um

Current Starved Inverter Chain

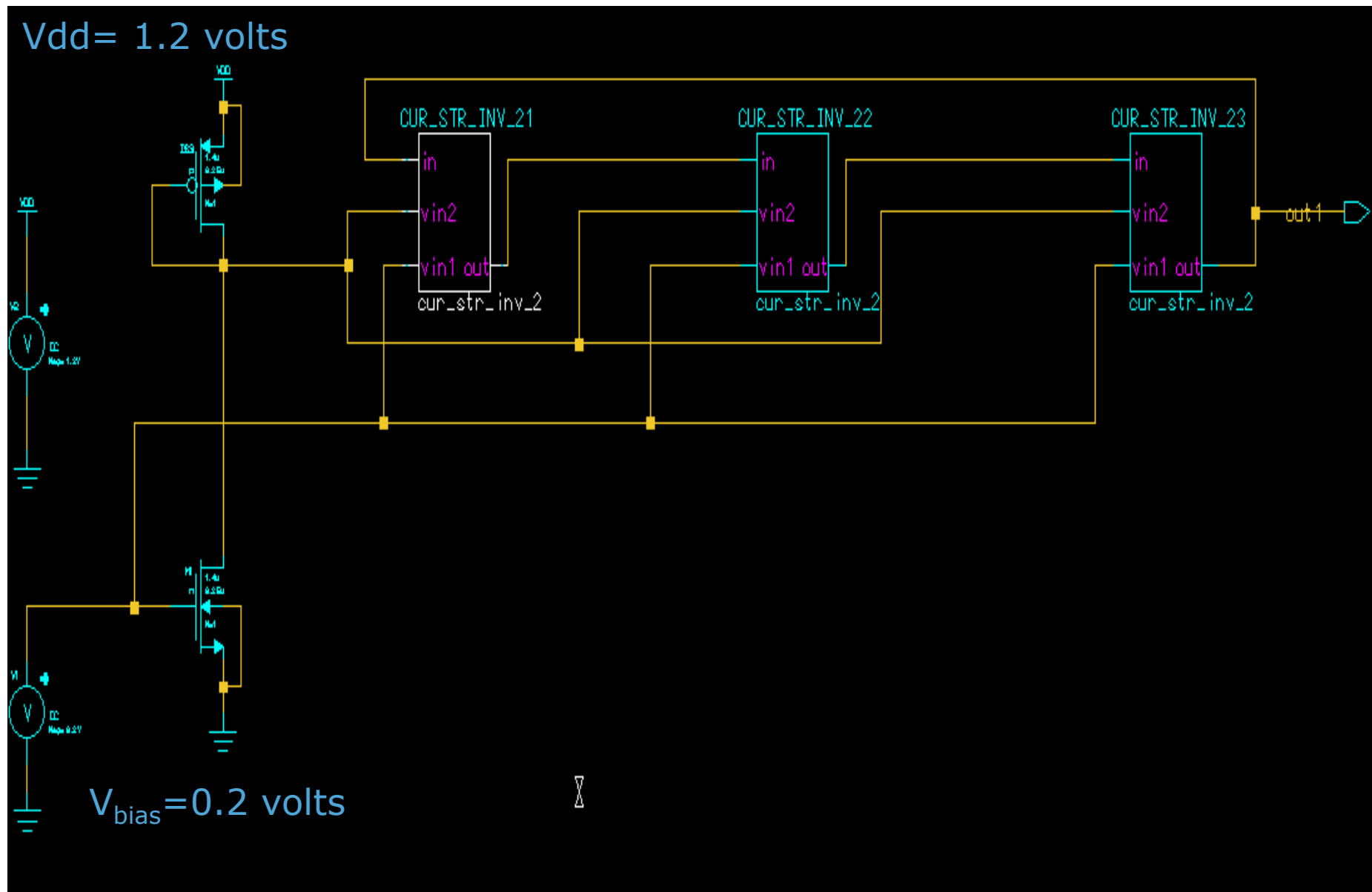


Current Starved Inverter Chain

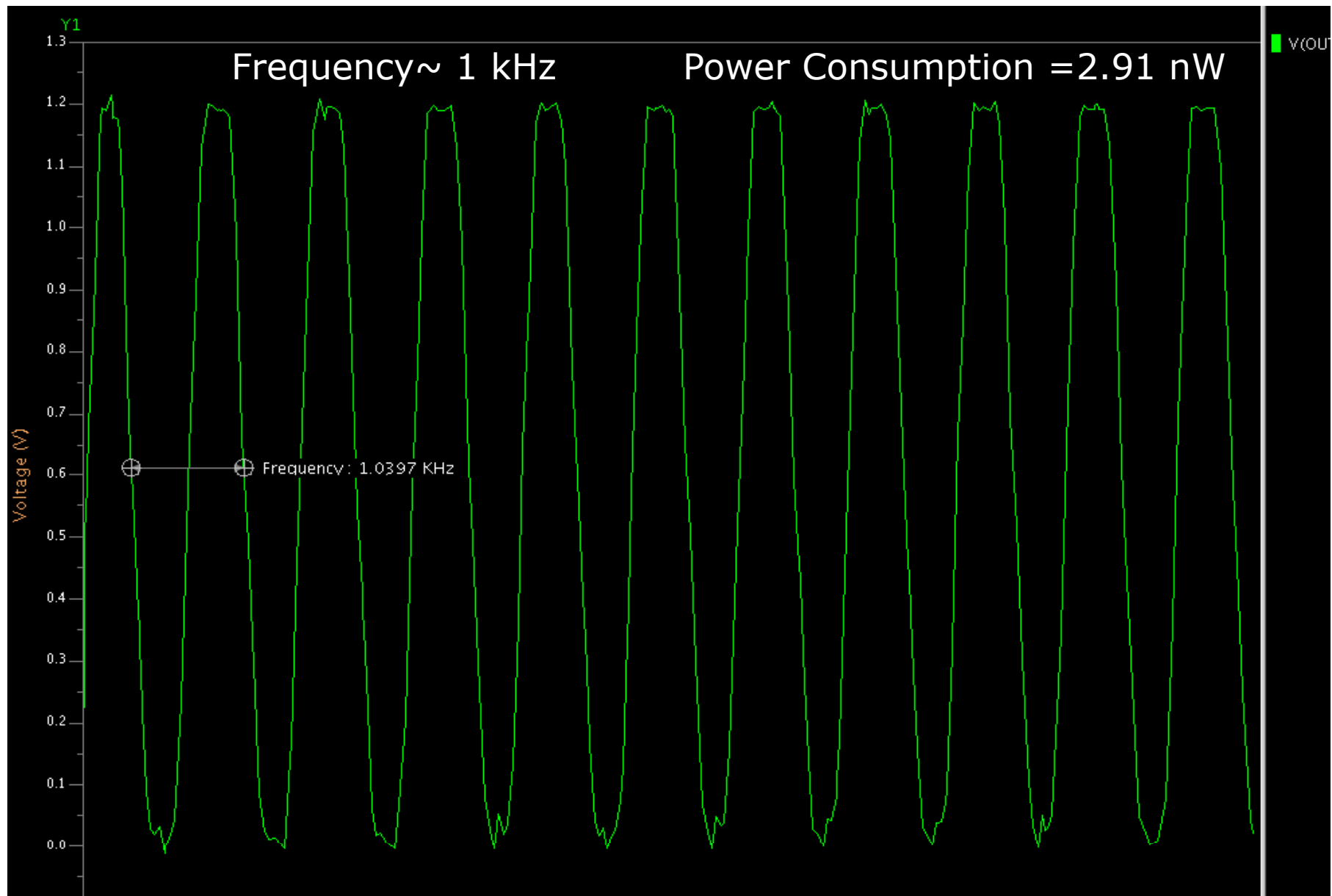

Current Starved Inverter Chain

Issue

- Voltage Sensitivity

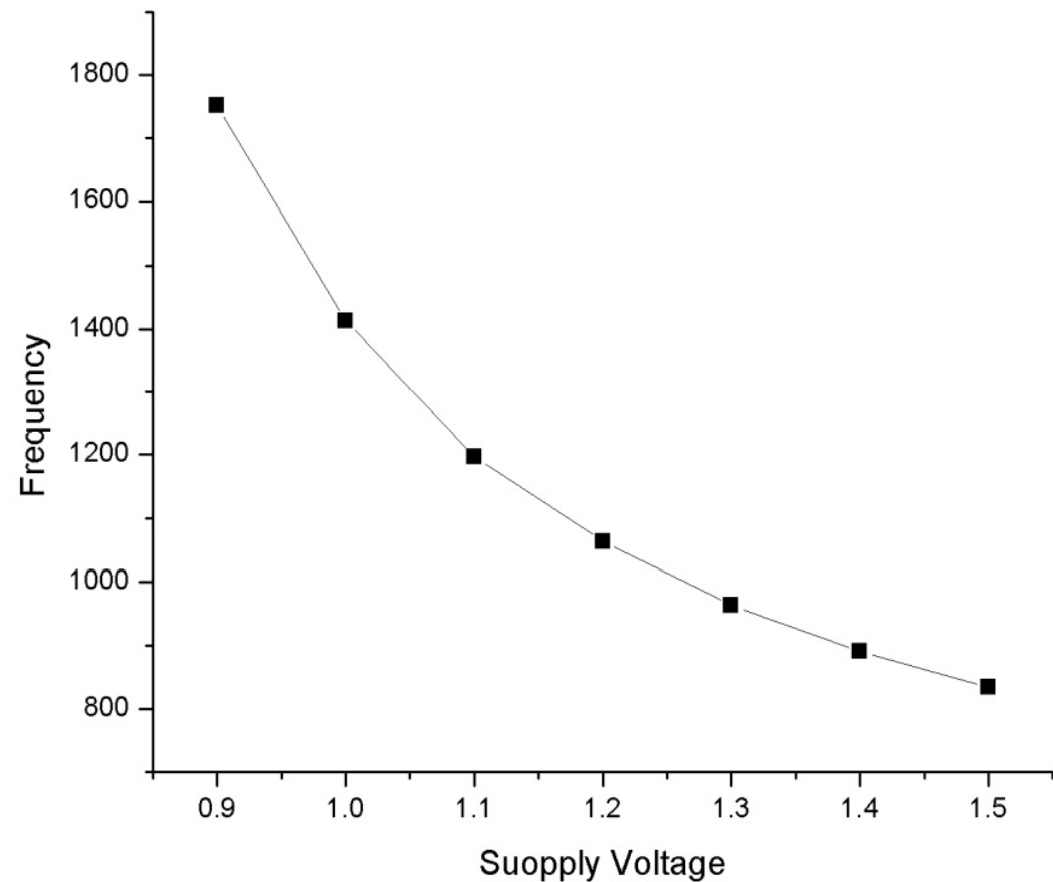


Outline


- ❑ Overview of Ring Oscillators
- ❑ Simple Inverter Chain
- ❑ Current Starved Inverter Chain
- ❑ **CMOS Thyristor Based Inverter**
- ❑ CMOS Thyristor with Footer
- ❑ Comparison
 - ❑ Voltage Sensitivity
 - ❑ Temperature Sensitivity
- ❑ References

CMOS Thyristor Based Inverter

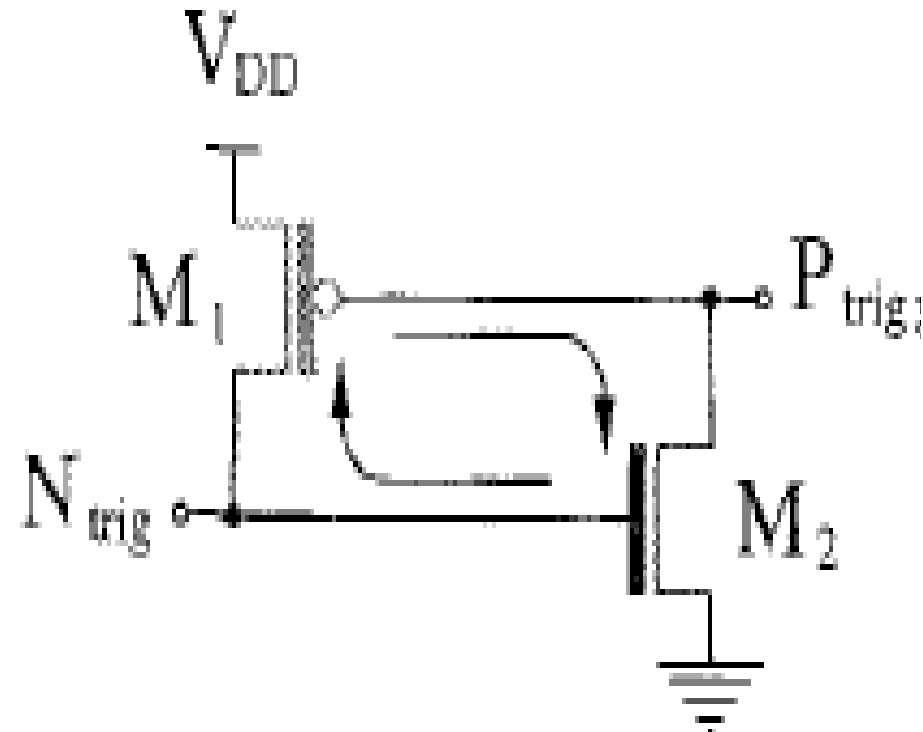
- Meta Stable Circuit
- Depend only on Leakage Current




CMOS Thyristor Based Inverter

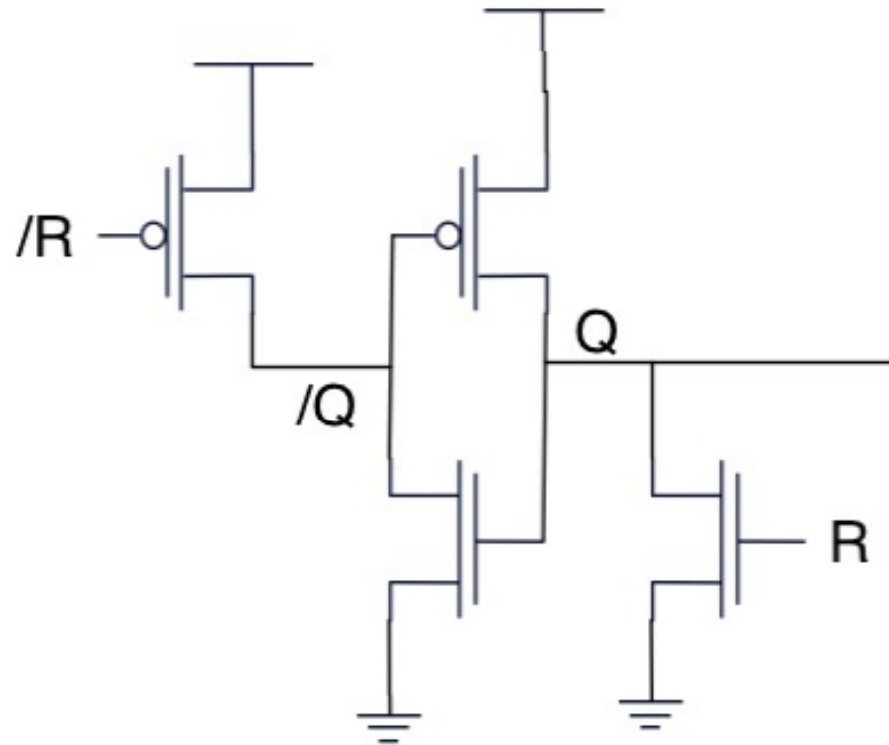


CMOS Thyristor Based Inverter

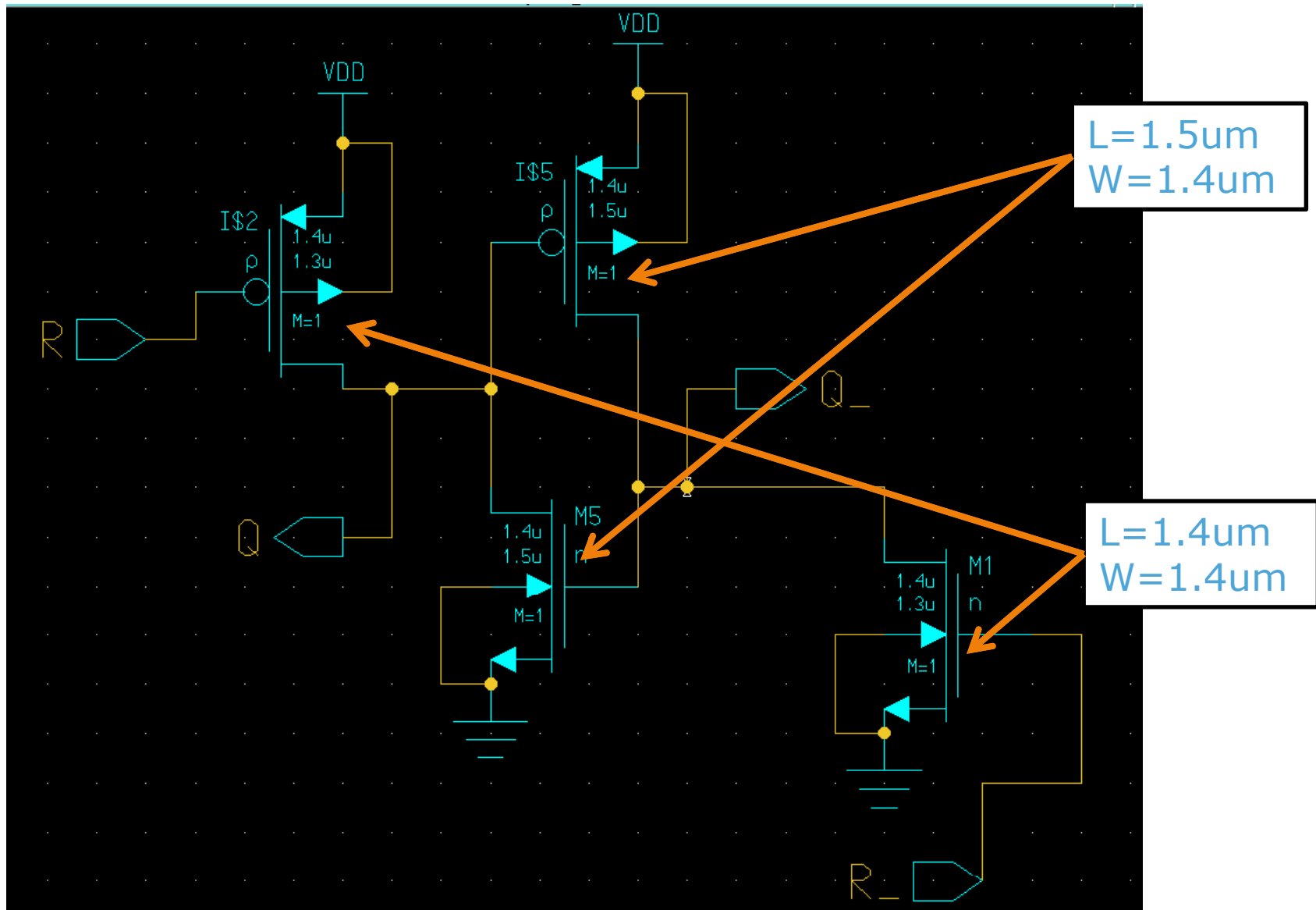

CMOS Thyristor Based Inverter

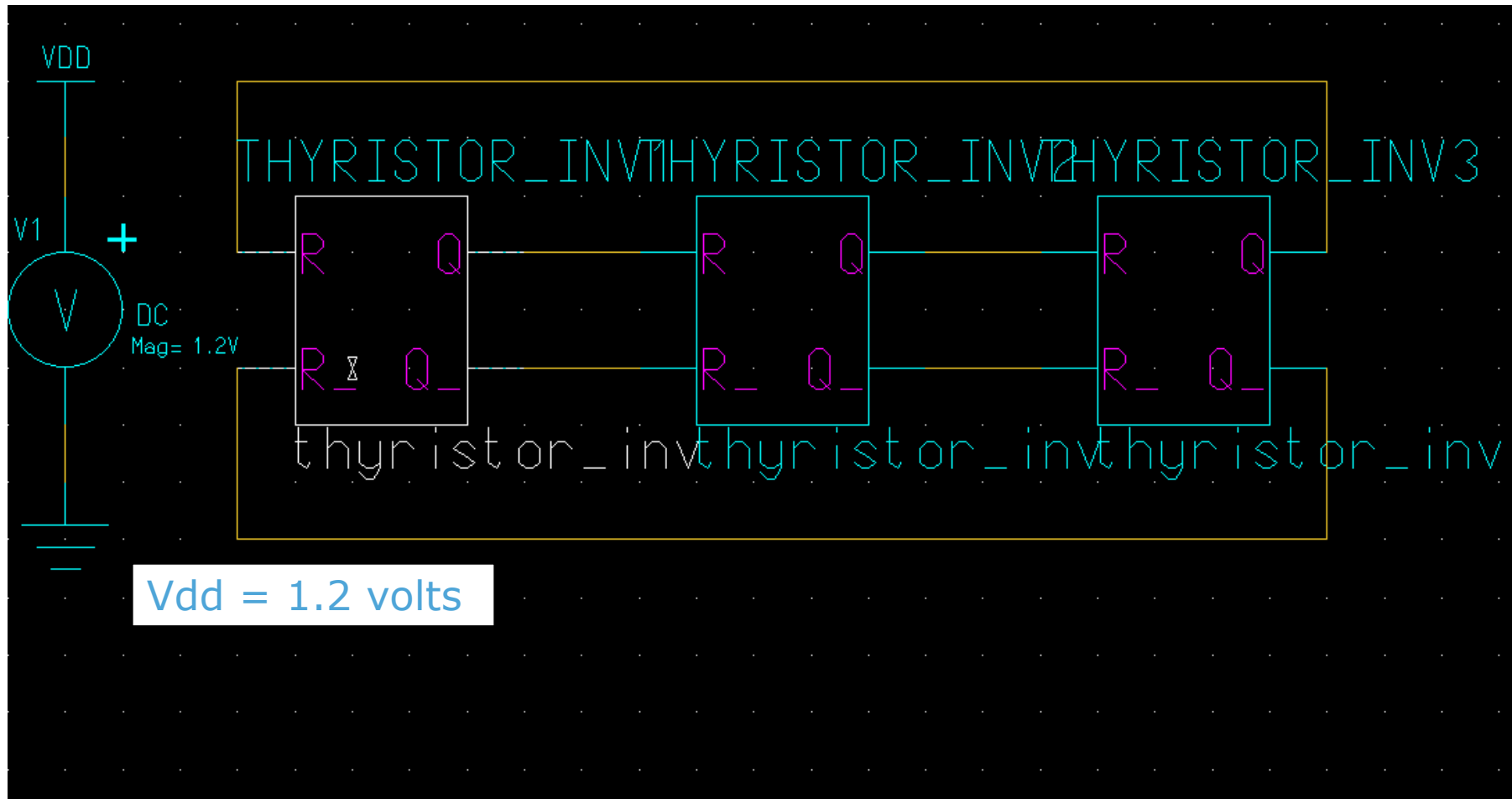


CMOS Thyristor Based Inverter

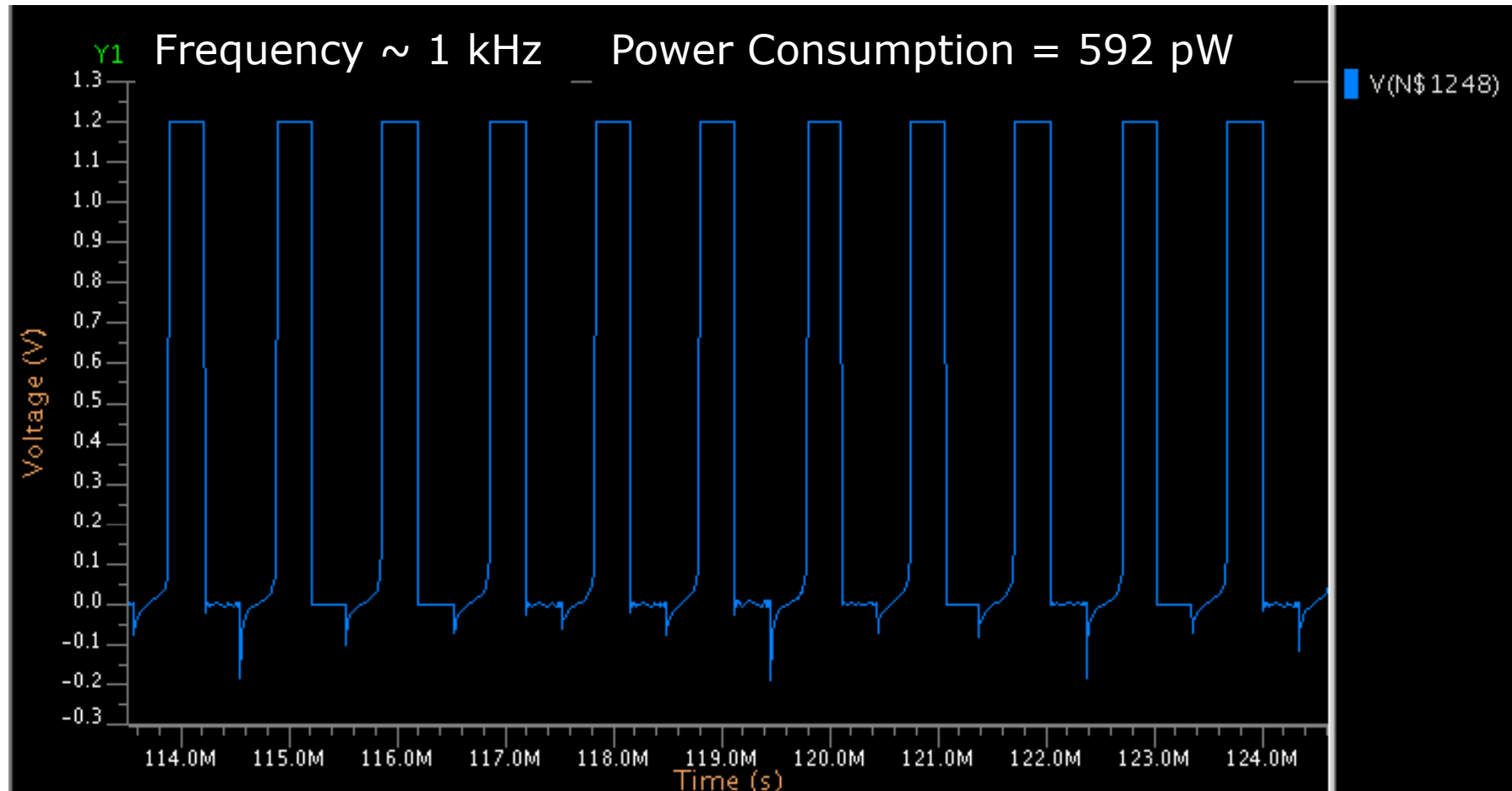


Outline

- ❑ Overview of Ring Oscillators
- ❑ Simple Inverter Chain
- ❑ Current Starved Inverter Chain
- ❑ CMOS Thyristor Based Inverter
- ❑ **CMOS Thyristor with Footer**
- ❑ Comparison
 - ❑ Voltage Sensitivity
 - ❑ Temperature Sensitivity
- ❑ References

CMOS Thyristor with Footer

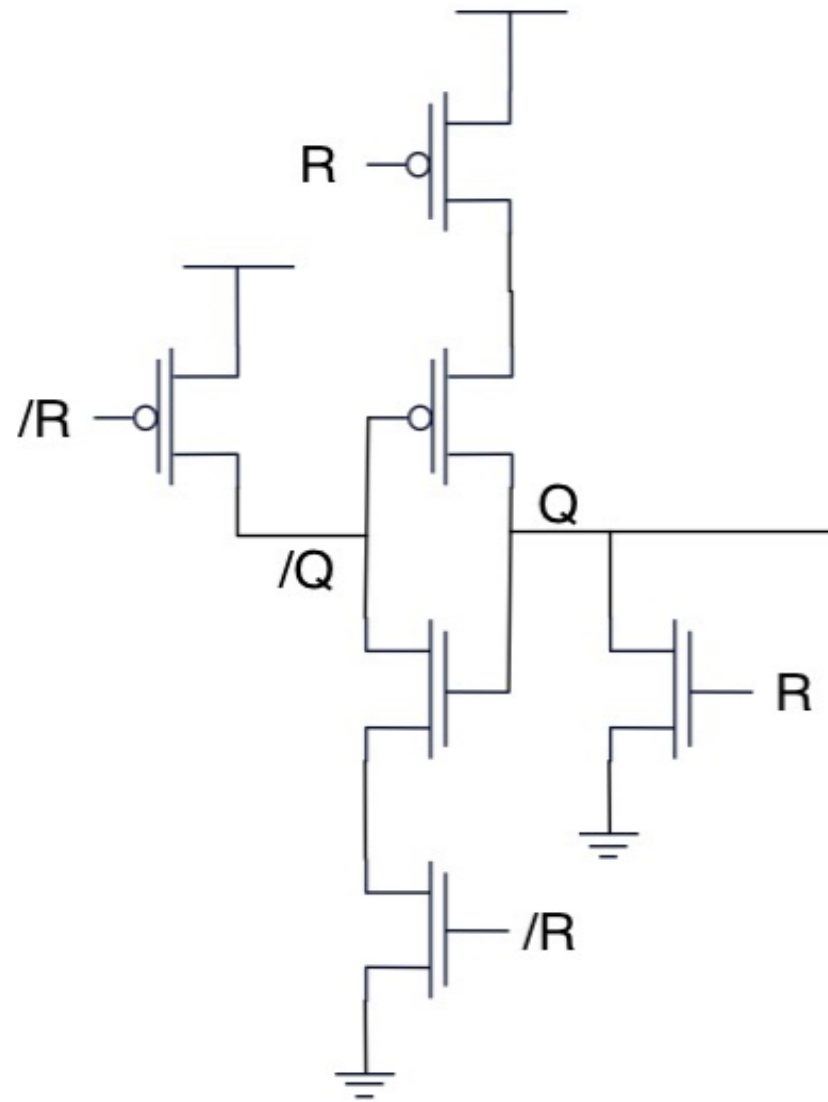


CMOS Thyristor with Footer

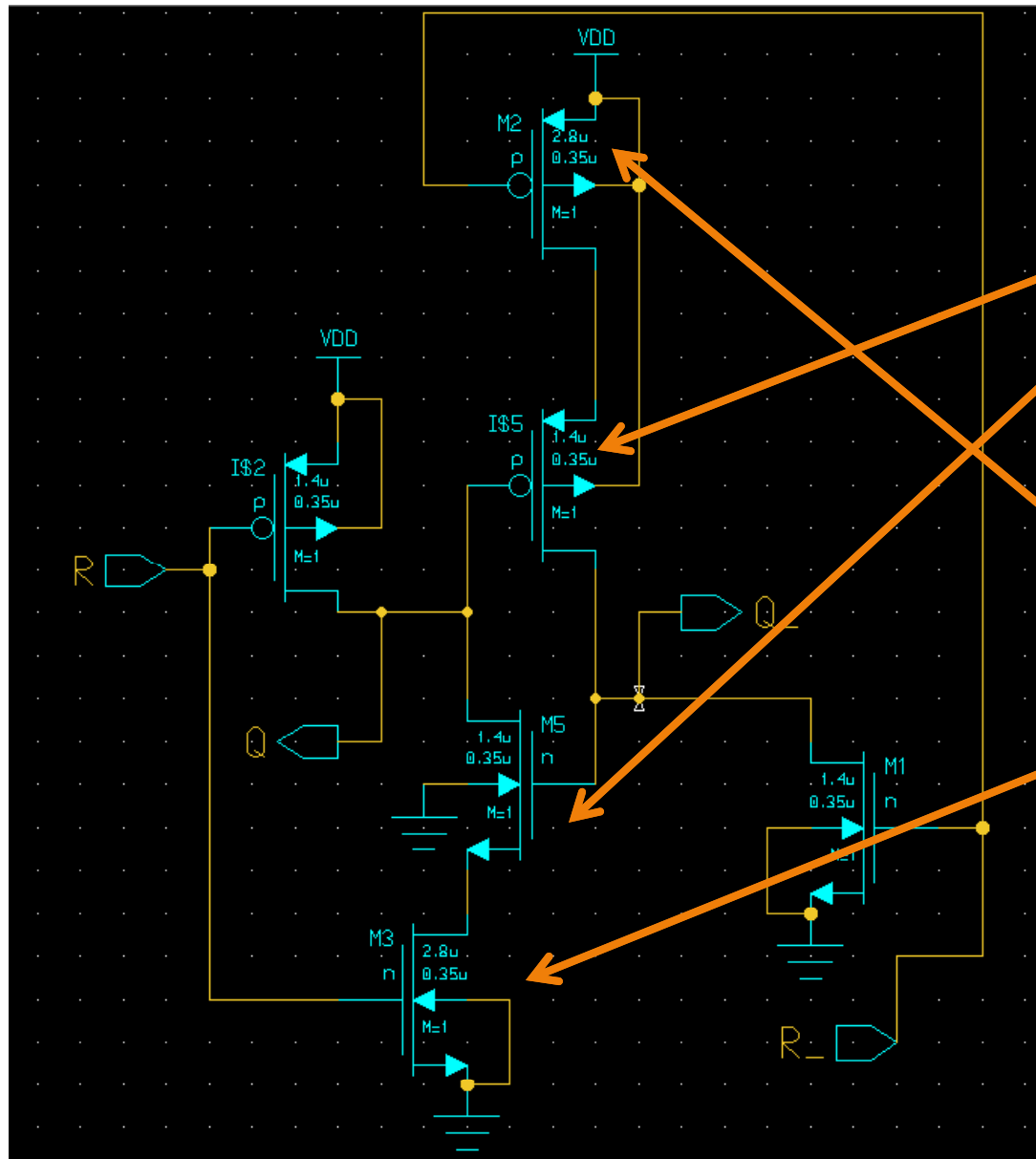


$L=0.35\mu\text{m}$
 $W=1.4\mu\text{m}$

$L=0.35\mu\text{m}$
 $W=2.8\mu\text{m}$

CMOS Thyristor with Footer

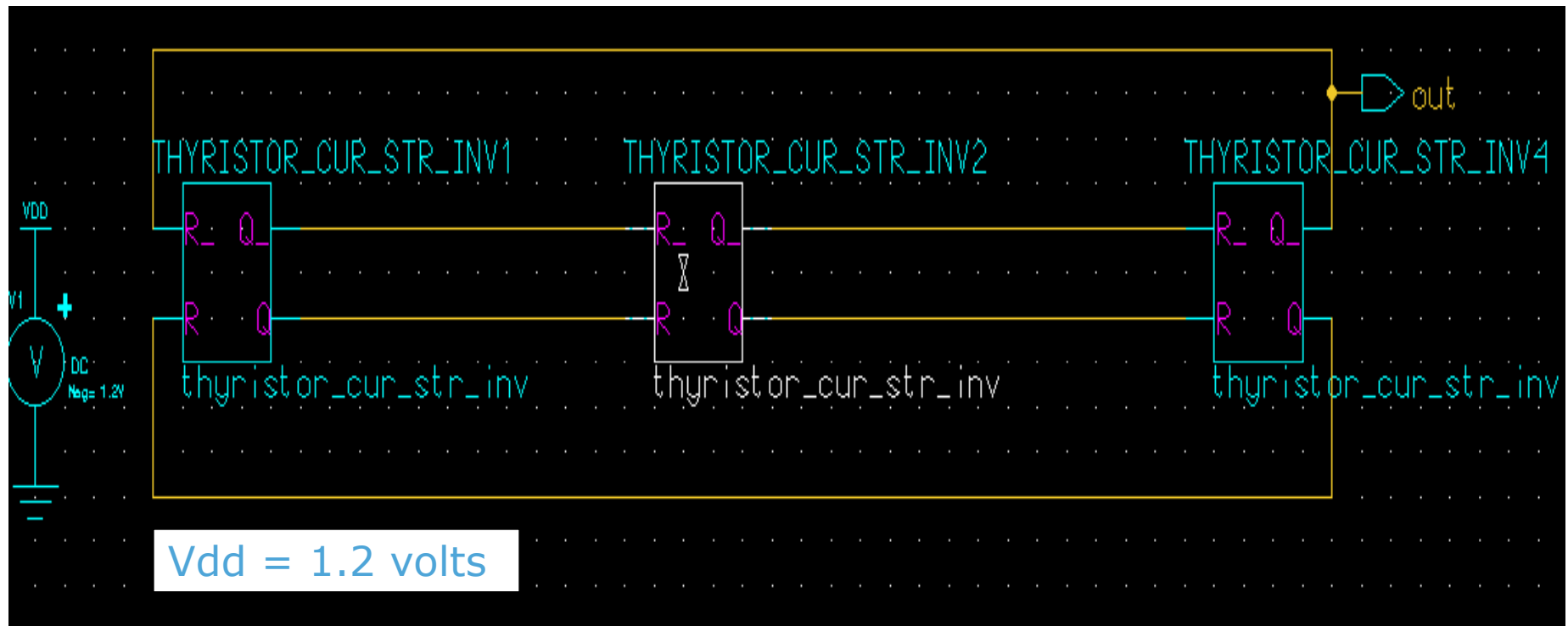

CMOS Thyristor with Footer

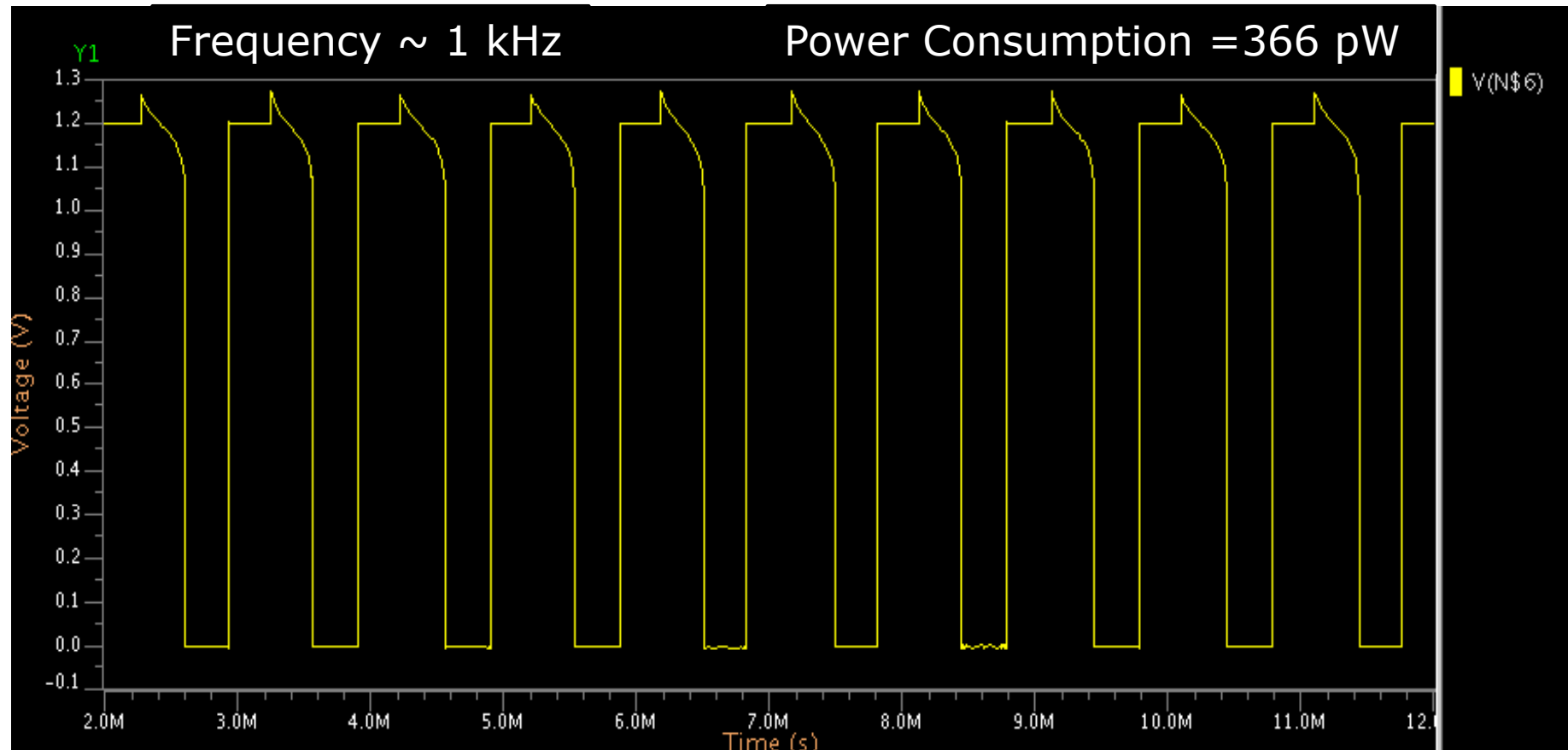


Outline

- ❑ Overview of Ring Oscillators
- ❑ Simple Inverter Chain
- ❑ Current Starved Inverter Chain
- ❑ CMOS Thyristor Based Inverter
- ❑ CMOS Thyristor with Footer
- ❑ Comparison
 - ❑ Voltage Sensitivity
 - ❑ Temperature Sensitivity
- ❑ References


Summary of Results

	No. Of Inverters	W		L		Power (nW)
SVT Inverter Chain	601	1.4um		35um		716 nW
Current Starved SVT $V_b=0.2V$	3	1.4um		9um (inverting transistor)	0.35um (starving transistor)	2.9 nW
CMOS Thyristor	3	1.4um		1.5um (inverting transistor)	1.3um (triggering transistor)	0.59 nW
CMOS Thyristor Footer	3	1.4um (inverting transistor)	2.8um (footer transistor)	0.35um		0.3 nW



Voltage Sensitivity

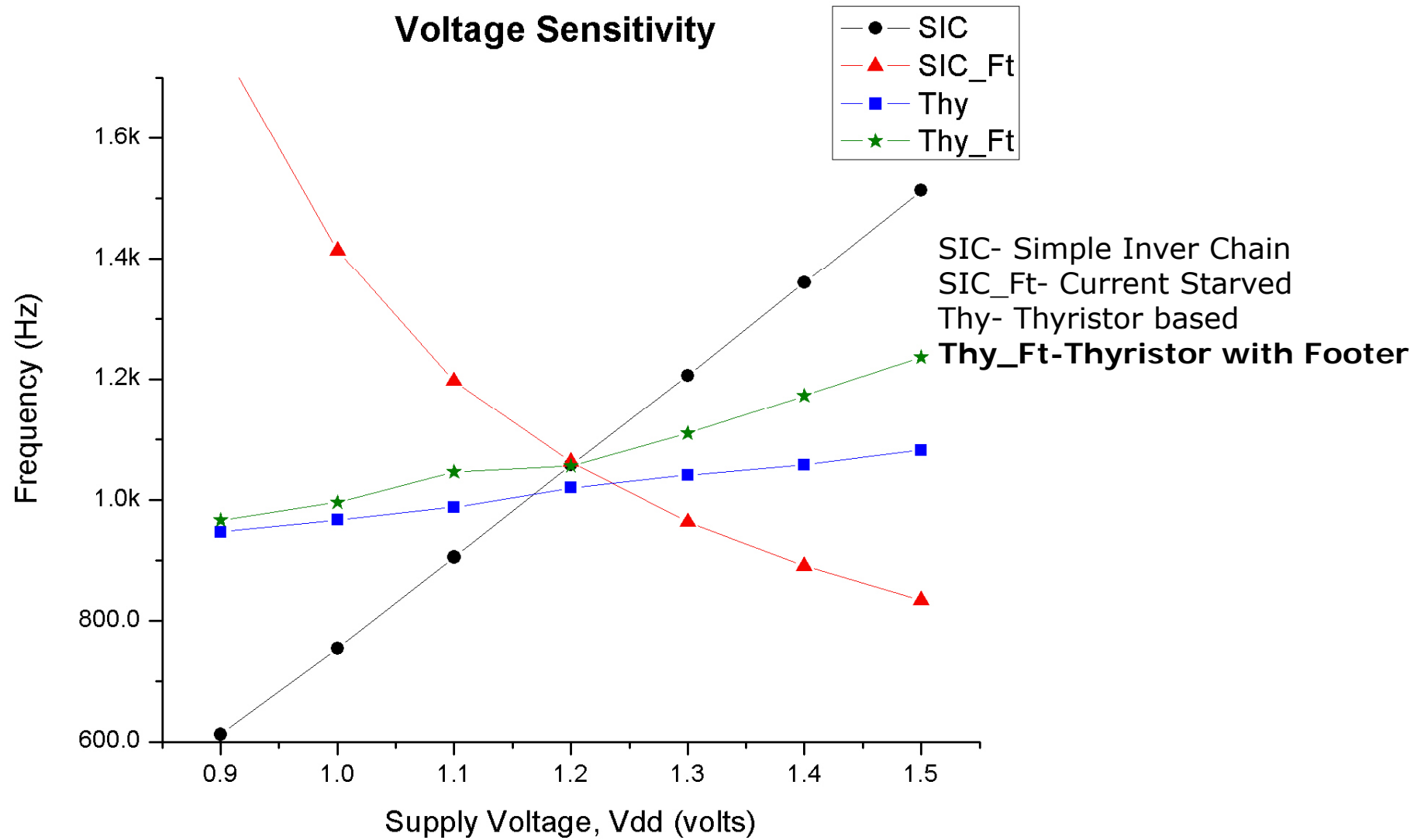

Temperature Sensitivity

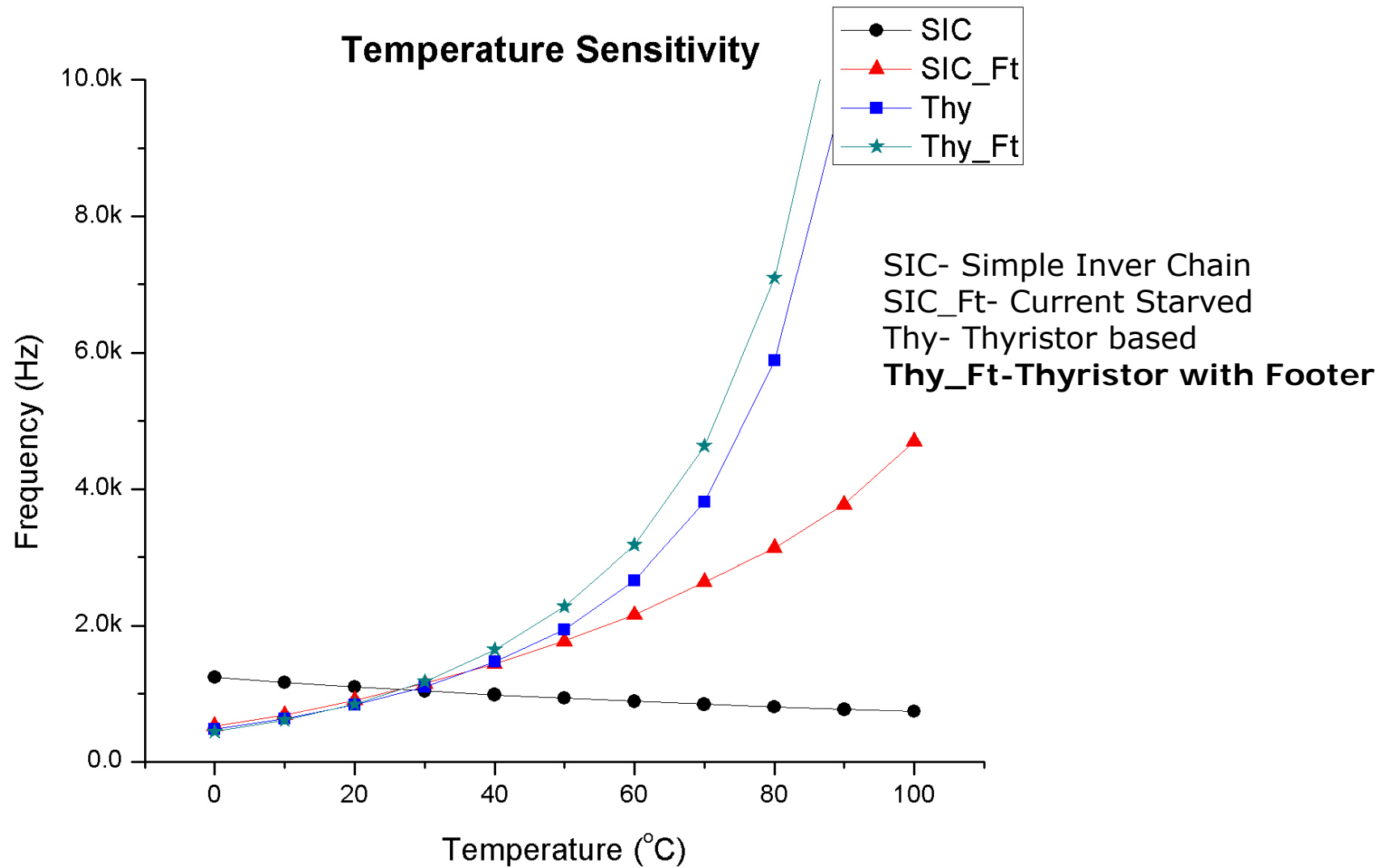

Temperature Compensation

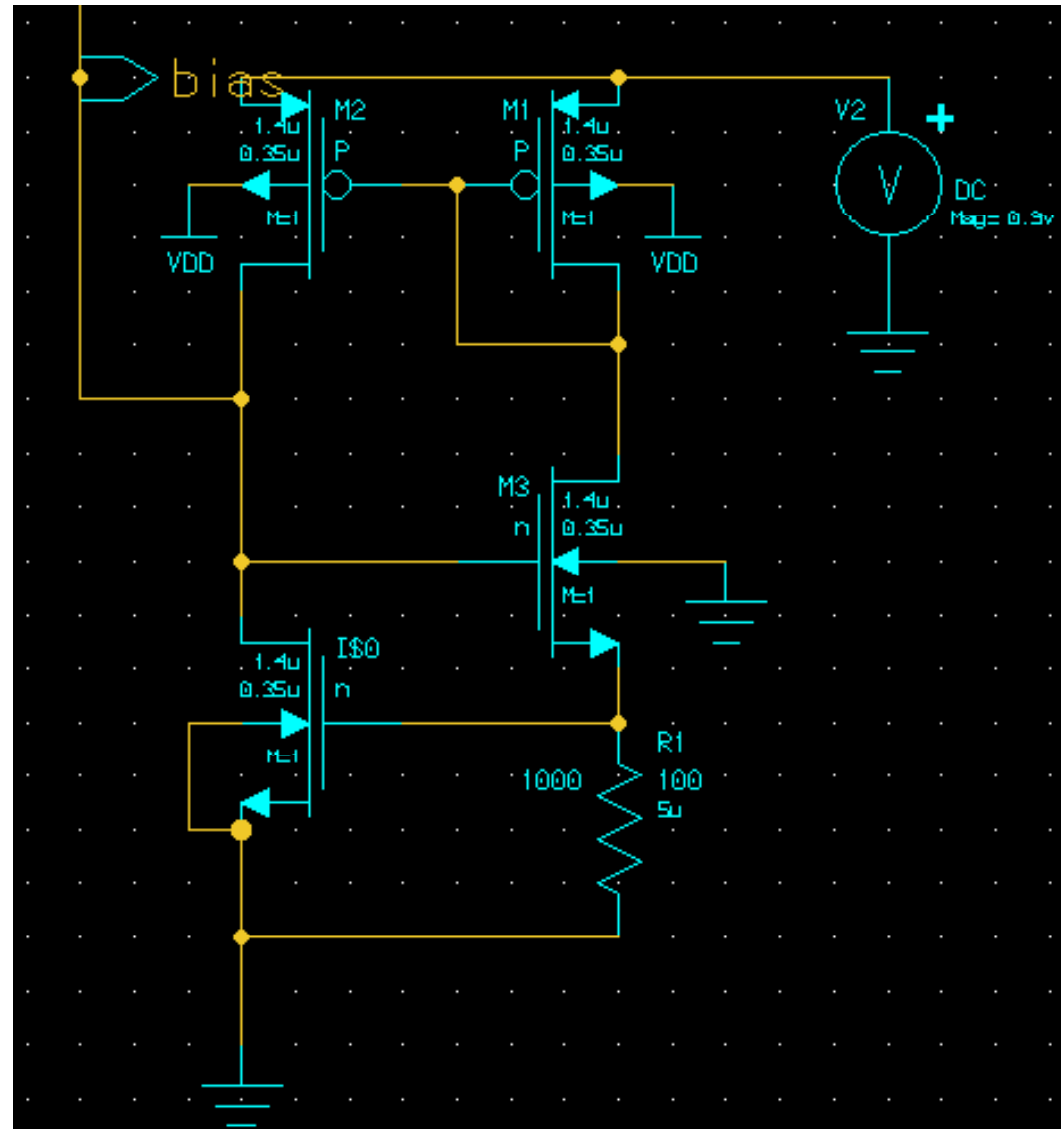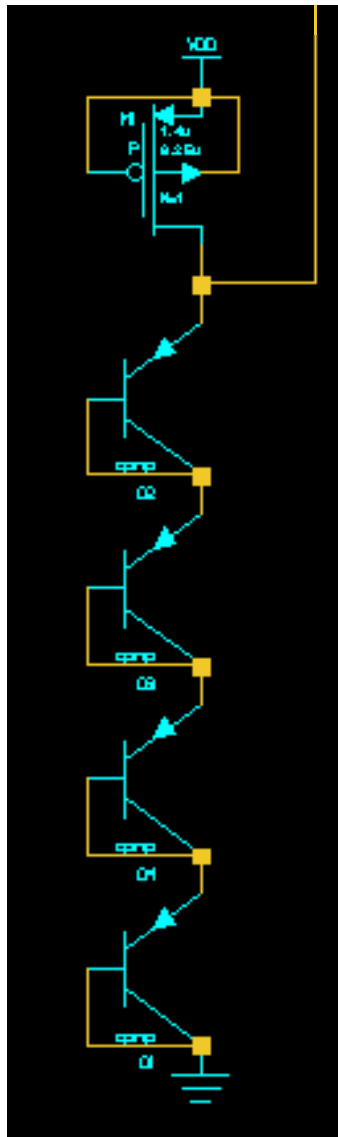

References

- **Research Papers**

1. G. Kim, M.K. Kim, B.C. Chang, W. Kim; “A Low Voltage, Low Power CMOS Delay Element”, IEEE journal of Solid-State Circuits, vol. 37, issue-7, July 1996, pp. 966-971.
2. J. Zhang, S.R. Cooper, A.R. Lapietra, M.W. Mattern, R.M. Guidash, E.G. Friedman; “A Low-Power Thyristor Based CMOS Programmable Delay Element”, ISCAS’04, Proceedings of 2004 International Symposium, May 2004, pp. 769-762.
3. K. Sundaresan, P.E. Ellen, F. Ayazi; “Process and Temperature Compensation in a 7-MHz CMOS Clock Oscillator”, IEEE journal of Solid-State Circuits, vol. 41, issue-2, Feb. 2006, pp. 433-442.

Thank you!